

Experiment - 1

Aim - Study of various measurement equipment listed below.

- a) To find the amplitude and frequency using CRO
- b) Study of multimeter.
- c) Bread Board
- d) Signal Generator
- e) DC voltage source

Components and Equipment's Required -

Cathode Rays, ~~Oscilloscope (CRO)~~, Signal Generator, resistance, capacitors, multimeter, bread board, CRO probes, testing probes and DC voltage source

Theory -

The block diagram shown in Fig. 1, explain how an oscilloscope works. Like a television screen, the screen of an oscilloscope consists of a Cathode Ray Tube (CRT) which is also called the heart of CRO. Although the size and shape are different, the operating principle is the same. Inside the tube is a vacuum. The electron beam emitted by the heated cathode at the rear end of the tube is accelerated and focused by one or more anodes, and strikes the front of the tube, producing a bright spot on the phosphorescent screen.

The electron beam is bent, or deflected, by voltages applied to two sets of plates fixed in the tube. The horizontal deflection plates or

Teacher's Signature _____

X plates produce side to side movement. As you can see, they are linked to a system block called the time base. This produces a saw tooth waveform. During the rising phase of the saw tooth, the spot is driven at a uniform rate from left to right across the front of the screen. During the falling phase, the electron beam returns rapidly from right to left, but the spot is 'blanked out' so that nothing appears on the screen. In this way, the time base generates the X-axis of the VT graph. The slope of the rising phase varies with the frequency of the saw tooth and can be adjusted, using the TIME/DIV control, to change the scale of the X-axis. Dividing the oscilloscope screen into squares allows the horizontal scale to be expressed in seconds, milliseconds or microseconds per division (s/DIV, ms/DIV, μ s/DIV). The signal to be displayed is connected to the input. The AC/DC switch is usually kept in the DC position (switch closed) so that there is a direct connection to the Y-amplifier. In the AC position (switch open) a capacitor is placed in the signal path. The capacitor blocks DC signal but allows AC signals to pass. The Y-amplifier is linked in turn to a pair of Y plates so that it provides the Y-axis of the Y-amplifier is linked in turn to a pair of Y-plates so that it provides the Y-axis of the VT graph.

The overall gain of the Y-amplifier can be adjusted, using the VOLTS/DIV control, so that the resulting display is neither too small nor too large, but fits the screen and can be seen clearly. The vertical scale is usually given in V/DIV or mV/DIV. The trigger circuit is used to delay the time base waveform, so that the same section of the input signal is

displayed on the screen each time the spot moves across. The effect of this is to give a suitable picture on the oscilloscope screen, making it easier to measure and interpret the signal.

changing the scales of the X-axis and Y-axis allows many different signals to be displayed. Sometimes, it is also useful to be able to change the position of the axes. This is possible using the X-POS and Y-POS controls. For example, with no signal applied, the normal trace is a straight line across the centre of the screen. Adjusting X-POS allows the zero level on the Y-axis to be changed, moving the whole trace up or down on the screen to give an effective display of signals like pulse waveforms which do not alternate between positive and negative.

Formula used

$$V(p-p) = X^* Y$$

$$V_m = V(p-p)/2$$

$$T = X^* Y$$

$$F = 1/T$$

Theory.

Cathode Ray Oscilloscope (CRO)

It consists of a cathode ray tube (CRT) which is also called the screen and shape are different, the operating principle is the same. Inside the tube is vacuum. The electron beam emitted by the heated cathode at the rear end of the tube is accelerated

Teacher's Signature _____

and focused by one or more anode and strikes the front of the tube, producing the bright spot on the phosphorescent screen.

Multimeter

A multimeter is an instrument that allows us to make multiple electrical measurements using the same tool. We can use it as a voltmeter to measure voltage, as an ammeter to measure current, as an ohm meter to measure resistance. There are two types of multimeter.

(i) Digital multimeter

They are superior to analogue multimeter because of their better accuracy in measurements, sensitivity to very small changes in input voltage and clear and easy to read displays.

(ii) Analog multimeter

Since digital multimeters need a power supply such as batteries. Also because they digitise the analog signals, multimeters can add noise. In addition, digital multimeters are not the best when it comes to testing semiconductor electronic parts.

Bread Board

A thin plastic board used to hold electronic components that are wired together used to develop prototype of electronic circuits wired together used to develop prototypes of electronic circuits, bread board can be used for failure jobs. They can be used to create one of a kind system but rarely become commercial products.

Teacher's Signature _____

Signal Generator.

Signal generator also called as a function generator useful in generating different types of wave form like sine wave, rectangular wave.

DC source or power supply

The power supply has an electrically floating output. This permits easy series or parallel connection with other power supply units to decrease supply voltage or current respectively. Basically, the power supply is constituted by rectifier, filters and basically the power supply is constitute by supply.

Observation Table

S.No	No. of vertical division (x)	Voltage / Division (x)	$V_{(P-P)} = X \cdot Y$ m (volt)	$V_m = V_{(P-P)} /$ m (volt)
1	5	2	6	3
2	4	2	8	4
3	6	2	12	6
4	2	2	4	2.

S.No.	No. of horizontal division (x)	Voltage / Division (y)	$T = X \cdot Y$ millisecond.	$F = 1/T$ (KHz)
1	4	0.5	2	0.5
2	1	0.5	0.5	2
3	2	0.5	1	1
4	5	0.5	2.5	0.4

Teacher's Signature _____

S.No.	Resistance	Theoretical Value	Practical Value
1	R_1	$10 \times 10^3 \pm 5\%$	9.98×10^3
2	R_2	$10 \times 10^1 \pm 5\%$	9.99×10^1
3	R_3	$10 \pm 5\%$	9.97
4	R_4	$10 \times 10^2 \pm 5\%$	9.9×10^2

Conclusion

These measurement equipments are highly useful and have their specific use which are used commonly in electronics. The study of multimeter breadboard, function generator and power supply is completed.

~~Q=25~~

Experiment - 2

Aim :-

Verification of ohm's law, Kirchoff's current law and voltage law.

Apparatus Required :-

Ohm's law, Kirchoff's law (Voltage and Current) are essential in the analysis of linear circuit. Kirchoff's law deal with the voltage and current in the circuit. Ohm's law relates voltage, current and resistances to one another. These three laws apply to resistive circuits.

1. Ohm's Law:-

Ohm's law is used to relate voltage to current and resistance. It states that voltage is directly proportional to current and resistance. This is stand mathematically

$$V = IR$$

V = Voltage in the current

I = current

R = Resistance

2. Kirchoff's Law:-

Kirchoff's Law Voltage (KVL) states that the sum of all voltage in a closed loop must be zero.

$$V_1 + V_2 - V_3 = 0$$

The equation holds true only if the passive sign convention is satisfied. In the case of KVL the passive sign convention states that when a positive node is connected while following a loop the voltage across the element is positive.

3. Kirchhoff's Current Law's:-

Kirchhoff's Current Law (KCL) deals with the current flowing into and out of a given node must equal to zero. KCL the passive sign convention deals with the direction of currents with respect to the node. Current entering the node must have opposite signs as those exiting the node. The passive sign convention with respect to KVL can also be applied to KCL.

4. Circuit Current Analysis:-

The current voltages and polarities were labelled as given in schematic, the current direction and voltage polarities have been assigned in such that the passive sign convention has been satisfied whenever possible.

Observation

KVL and KCL circuits are analyzed and the values of different parameters are mentioned.

Voltage V(v)	Resistance R (KΩ)	$I = V/R$
5V	1KΩ	$I = \frac{5V}{1K\Omega} = 5mA$

Voltage of resistor when measured with multimeter = 5V

V_{R_1}	V_{R_2}	$I_1 = \frac{V}{R_{eq}}$	$I_2 = \frac{V_{R_1}}{R_1}$	$I_3 = \frac{V_{R_2}}{R_2}$	$I_2 + I_3$
5.1	5.1	?	10.2	5.1	5.1 ?

: $I_1 \approx I_2 + I_3$

V_s	V_{R_1}	V_{R_2}	$V_s = V_{R_1} + V_{R_2}$	<u><u>V_mf</u></u>
5V	+2.56	2.54	5.1	—

$V_s \approx V_{R_1} + V_{R_2}$

Calculation

1) $I = \frac{V}{R} = \frac{5V}{1K\Omega} = 5mA$

2) $R_1 = R_2 = 1K\Omega$

$$R_{eq} = \frac{1 \times 1}{1+1} = \frac{1}{2} = 0.5 K\Omega$$

$$I_1 = \frac{V}{R_{eq}} = \frac{5}{0.5} = 10mA$$

$$I_2 = \frac{V_{R_1}}{R_1} = \frac{5.1}{1K\Omega} = 5.1mA$$

Teacher's Signature _____

$$I_3 = \frac{V_{R_2}}{R_2} = \frac{5.1}{1\text{ k}\Omega} = 5.1 \text{ mA}$$

$$I_2 + I_3 = 10.2 \text{ mA} = I_1, \quad I_3 = 5.1 \text{ mA}$$

$$I_1 = I_2 + I_3$$

3) $R_1 = 1\text{ k}\Omega, R_2 = 1\text{ k}\Omega$

$$R_{\text{eq}} = \frac{1 \times 1}{1+1} = \frac{1}{2} = 0.5 \text{ k}\Omega$$

$$V_s = 5 \text{ V}$$

$$V_1 = 2.56 \text{ V}; \quad V_2 = 2.54 \text{ V}$$

Clearly, $V_s = V_1 + V_2$.

Result

(a) The calculated and measured values match ohm's law, Kirchhoff's current law and Kirchhoff's voltage law have been verified successfully.

Experiment - 3

Aim : To study and verification of Thvenin's Theorem.

Apparatus Required : Bread-board, Multi-meter, Resistance, Voltage/Current Source, Connecting wires, etc.

Theory :

(a) Thvenin's Theorem: It states that "Any linear circuit containing several voltages and resistance can be replaced by just one single voltage in series with a single resistance connected across the load". In other words, it is possible to simplify any electrical circuit, no matter how complex, to an equivalent two-terminal circuit with just a single constant voltage source in series with a resistance (or impedance) connected to a load as shown below.

Simple steps to analyse electronic circuit given in Fig. through Thvenin's Theorem.

1. Open the load resistor
2. Calculate / measure the open circuit voltage. This is the Thvenin's voltage (V_{th})
3. Open current source and short the voltage sources.
4. Calculate / measure the open circuit resistance. This is the Thvenin's resistance (R_{th})
5. Now, Redraw the circuit with measured open circuit voltage (V_{th}) in step (2) as voltage source and measured the open

Teacher's Signature _____

With the help of Thévenin's theorem we can analyze the circuit.

Let us consider the circuit shown in Fig. 3.1.

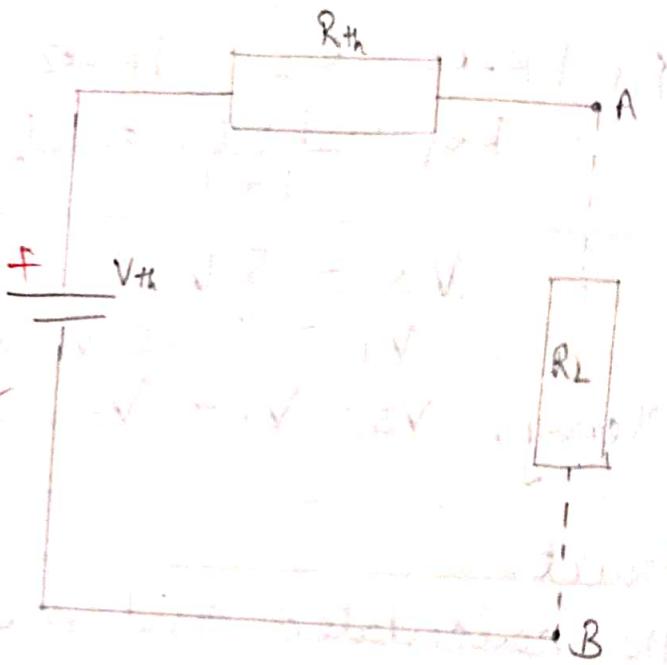
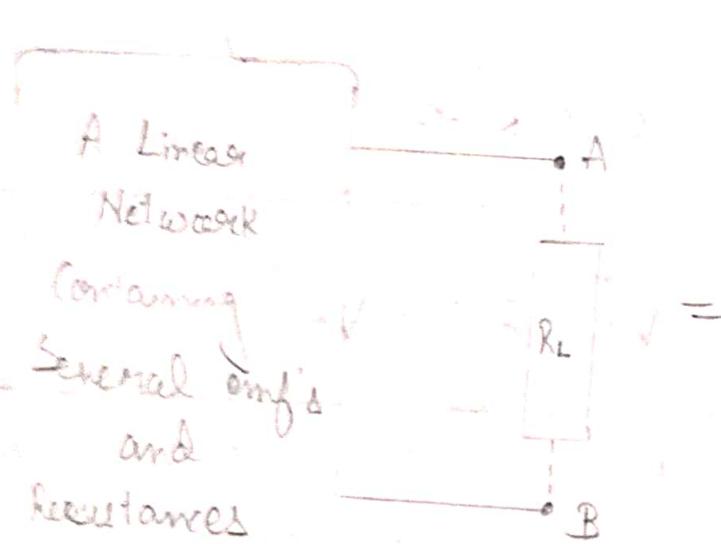


Fig. 3.1 Thévenin's Equivalent Circuit

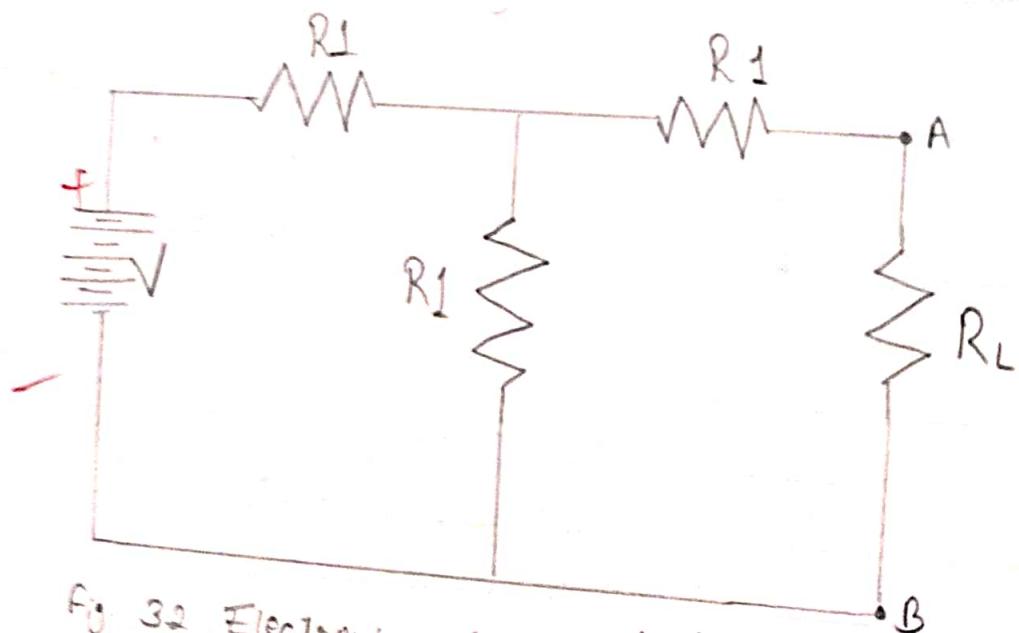


Fig. 3.2 Electronic circuit to be analyzed through
Thévenin's Theorem

circuit resistance (R_{th}) in step (4) as a series resistance and connect the local load resistor which had been removed in step (1). This is the equivalent Thvenin circuit of that linear electric network or complex circuit which had to be simplified and analyzed by Thvenin's Theorem.

Formula used :-

$$V_{oc} = IR_3$$

$$I = V / (R_1 + R_3)$$

$$V_{oc} \text{ or } V_{th} = V * R_3 / (R_1 + R_3)$$

$$R_{th} = R_2 + \frac{R_1 * R_3}{R_1 + R_2}$$



Observation Table.

S.No	Theoretical values	Experimental values
------	--------------------	---------------------

R_{th} ($k\Omega$)	V_{th} (v)	I_L (mA)	R_{th} ($k\Omega$)	V_{th} (v)	I_L (mA)
1 2.102	1.784	0.26	2.101	1.846	0.12

S.No.	Theoretical ($k\Omega$)	Experimental ($k\Omega$)
R_1	1.769 $k\Omega$	1.8
R_2	1.471 $k\Omega$	1.5
R_3	0.982	1
R_4	4.82	4.7

Teacher's Signature _____

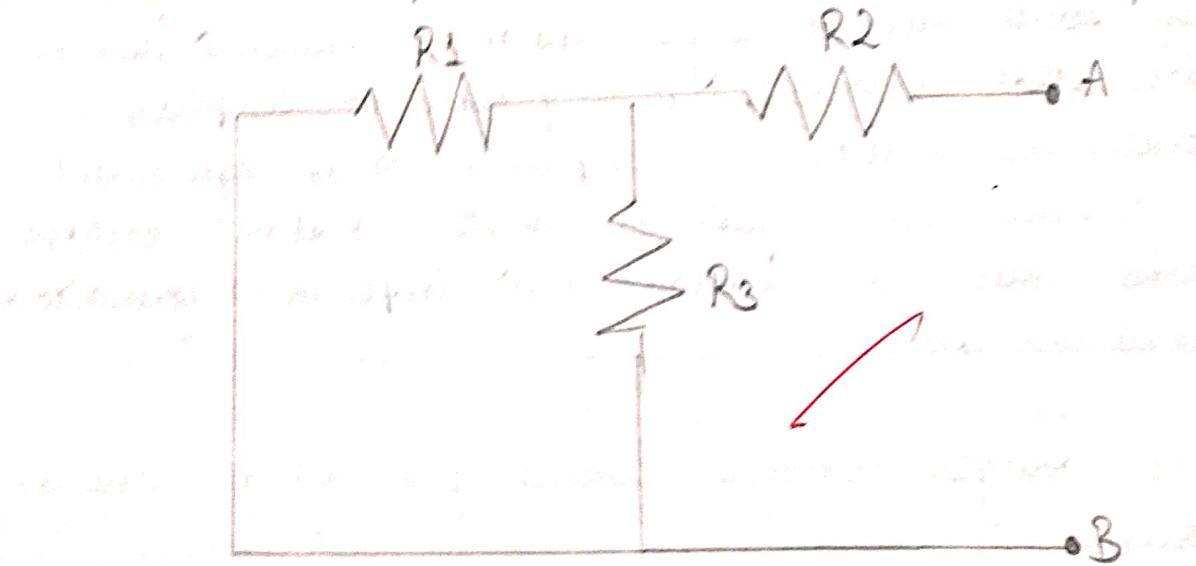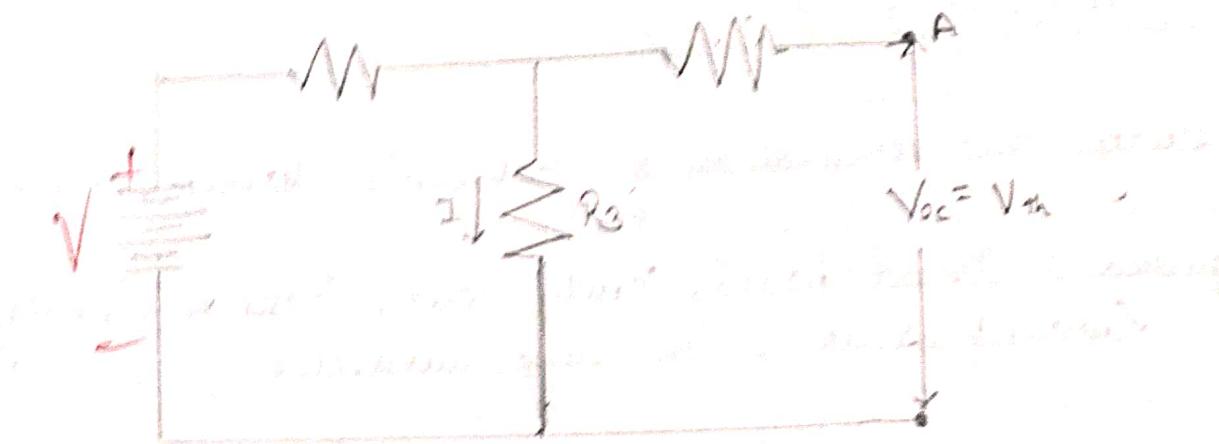

Calculation

$$1) R_{TH} = \frac{R_1 \cdot R_3}{R_1 + R_3} + R_2$$

$$= \frac{1.769 \times 0.982}{1.769 + 0.982} + 1.971$$

$$= 2.102 \text{ k}\Omega$$

$$2) V_{TH} = \frac{V_s}{R_1 + R_3} \times R_3$$

$$= \left(\frac{5}{1.769 + 0.982} \right) 0.982$$

$$= 1.784 \text{ V}$$

$$3) I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{1.784}{2.102 + 4.82}$$

$$= 0.26 \text{ mA}$$

Result

~~09~~ Since Theoretical and practical values of Thevenin's theorem
~~are~~ almost the same. It is verified.

Experiment - 4

Aim

Study and perform superposition theorem.

Apparatus Required

DC power supply (+5V, +8V), resistances, multimeter, breadboard, connecting wires.

Theory

Superposition theorem states that if more than one source acts simultaneously in an electric circuit, then the current through any one of the branches of the circuit is the summation of currents which would flow through the branch for each source, keeping all the other sources dead.

Formula used.

$$1) i_1' = \frac{V_1}{R_1 + R_2 + R_3}$$

$$2) i_2' = \frac{i_1' \cdot R_3}{R_2 + R_3}$$

$$3) i_3' = \frac{i_1' R_2}{R_2 + R_3}$$

$$4) i_2'' = \frac{V_2}{R_2 + R_1 \cdot R_3}$$

$$5) i_1'' = \frac{i_2'' \cdot R_1}{R_1 + R_3}$$




$$6) i_3'' = \frac{i_2'' - R_1}{R_1 + R_3}$$

$$7) i_3 = i_1'' + i_2''$$

$$8) i_1 = i_1' - i_1''$$

$$9) i_2 = i_2'' - i_2'$$

Circuit Diagram

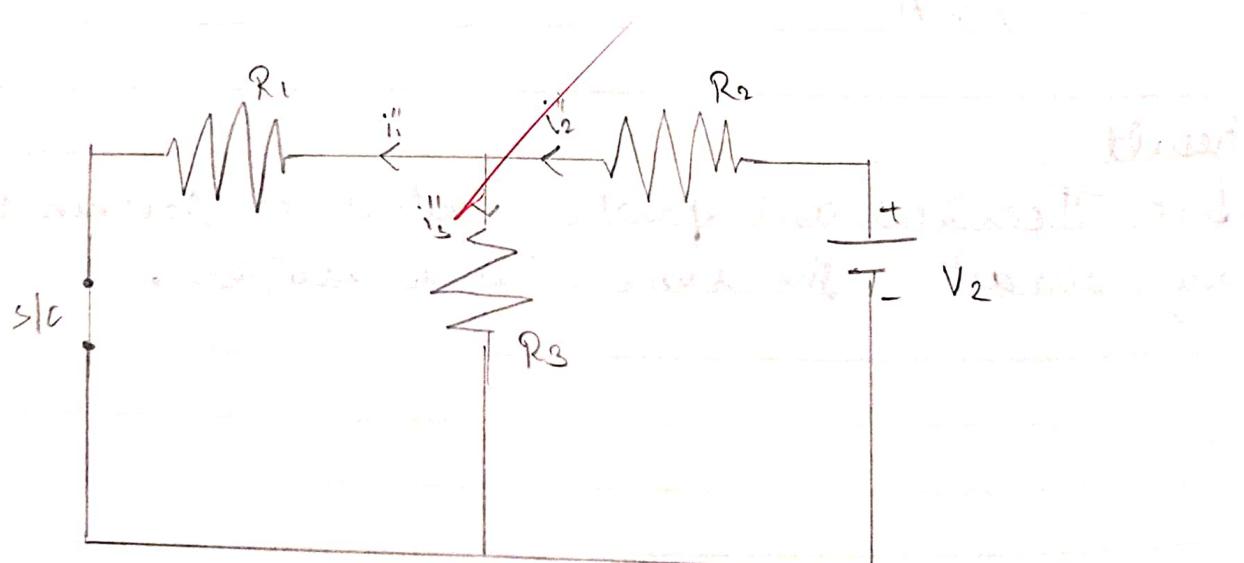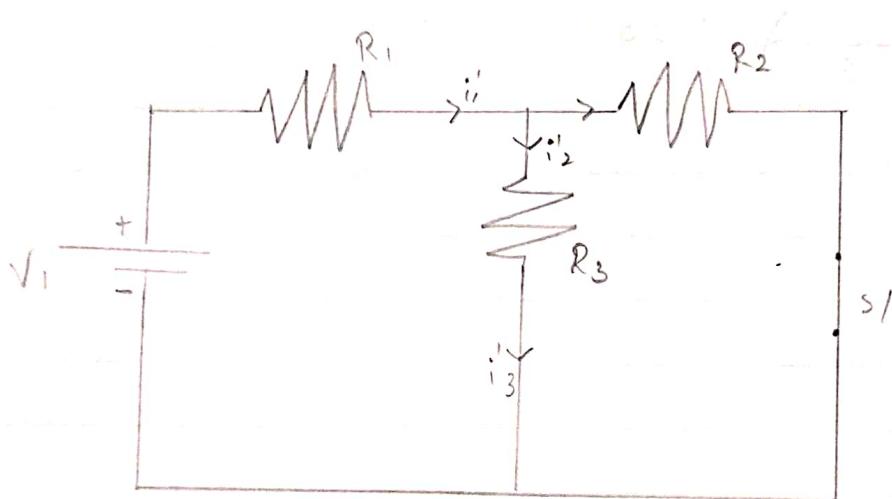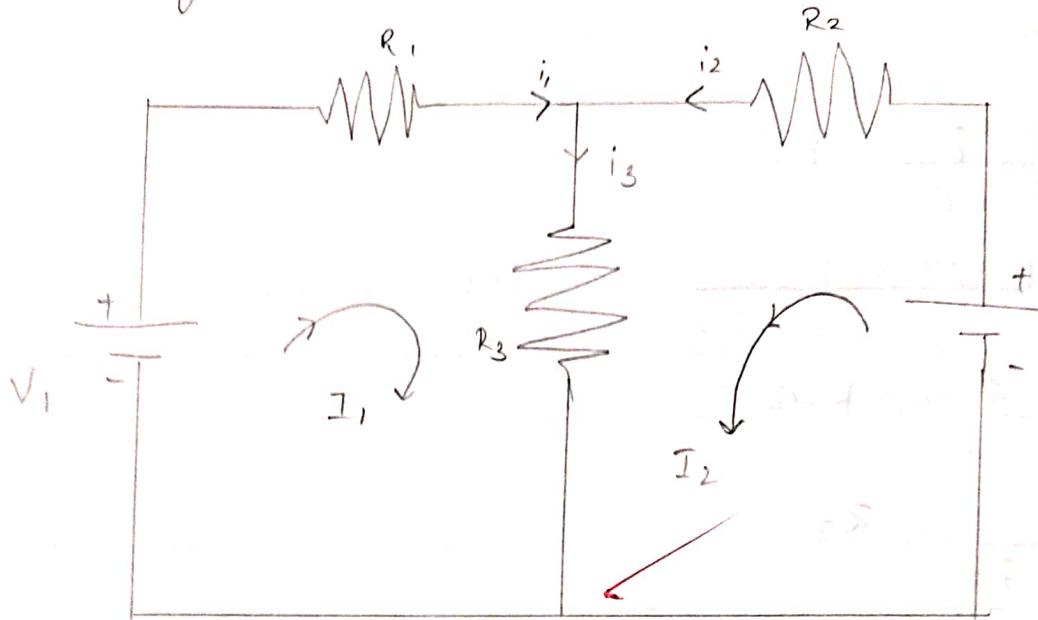

Calculation

$$1) i_1'' = \frac{V_1}{R_1 + R_2 + R_3} = \frac{5}{0.979 + (3.23 \times 9.84)} = \frac{5}{0.979 + 24.31} \\ = \frac{5}{3.23 + 9.84} = 1.4659 \text{ mA}$$

$$2) i_2' = \frac{i_1' \cdot R_3}{R_2 + R_3} = \frac{1.4659 \times 9.84}{3.23 + 9.84} = \frac{14.424}{13.07} \\ = 1.1035 \text{ mA}$$

$$3) i_3' = \frac{i_1' \cdot R_2}{R_2 + R_3} = \frac{1.4659 \times 3.23}{9.84 + 3.23} = \frac{4.7350}{13.07} \\ = 0.3622 \text{ mA}$$

$$4) i_2'' = \frac{V_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} = \frac{5}{3.23 + \left(\frac{0.979 \times 9.84}{0.979 + 9.84} \right)} = \frac{5}{3.23 + 0.890} \\ = 1.2134 \text{ mA}$$

$$5) i_1'' = \frac{i_2'' \cdot R_3}{R_1 + R_3} = \frac{1.2134 \times 9.84}{0.979 + 9.84} = \frac{11.9405}{10.819} \\ = 1.1036 \text{ mA}$$

$$6) i_3'' = \frac{i_2'' \cdot R_1}{R_1 + R_3} = \frac{1.2134 \times 9.79}{0.979 + 9.84} = \frac{11.9405}{10.819} = 1.1036 \text{ mA}$$

Observation

Desi Observed Current (mA) and Voltage (V)

i_1'	i_2'	i_3'	i_1''	i_2''	i_3''
1.469	1.108	0.362	1.107	1.219	0.110
V_1'	V_2'	V_3'	V_1''	V_2''	V_3''
1.439	3.58	3.57	1.084	3.94	1.083

Theoretical Value (mA)

Observed Value (mA)

i_1	i_2	i_3	i_1	i_2	i_3
0.3623	0.1099	2.317	0.361	0.109	2.115

$$7) i_3 = i_1'' + i_2'' \\ = 1.1036 + 1.2134 \\ = 2.317 \text{ mA}$$

$$8) i_1 = i_1' - i_1'' \\ = 1.4659 - 1.1036 \\ = 0.3623 \text{ mA}$$

$$9) i_2 = i_2'' - i_2' \\ = 1.2134 - 1.1035 \\ = 0.1099 \text{ mA}$$

Result

Superposition theorem has been verified successfully

1c
12.18.92 ✓

Experiment - 5

Aim

Verification of maxima for power transfer theorem.

Apparatus

Resistance, Pot, Multimeter, Voltage source (10 V).

Theory

The maximum power transfer theorem states that to obtain maximum external power from a source with a finite internal resistance, the resistance of the load must equal to the resistance of the source as viewed from its output terminal.

Formula Used:



$$\text{i) } I_L = \frac{V_L}{R_L} \quad (\text{Ohm's Law}).$$

$$\text{ii) } P = V_L I_L.$$

$$\text{iii) } P_m = \frac{V^2}{4 R_{th}}$$

Observation

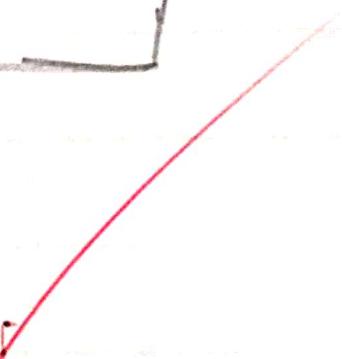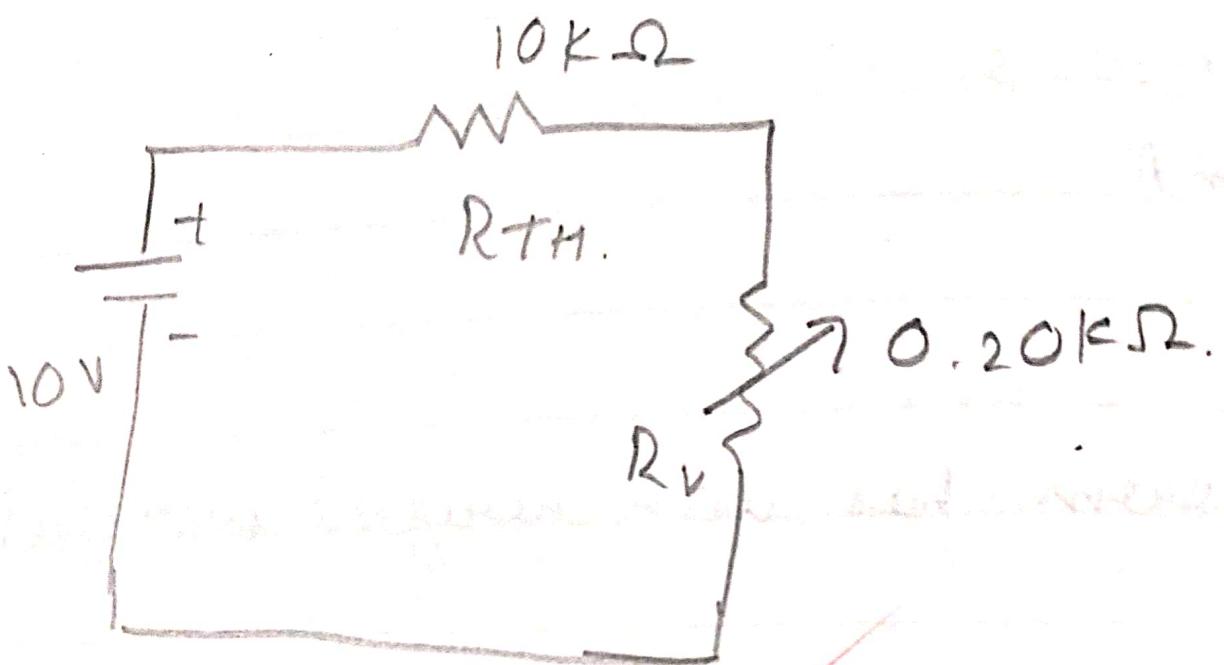Value of P_m showed in table 1 and shown in graph.



Observation Table.

S.No	R_{th} (Ω)	R_L (Ω)	V_L (V)	$R_L = V_L I_L$ (mW)	$P_{max} = \frac{V^2}{4R_L}$ (mW)
1	2	1.65	1.36		
2	3	2.48	2.05		
3	4	2.90	2.10		
4	6	3.7	2.39		
5	8	4.51	2.54		
6	10	5.09	2.59		2.5
7	12	5.53	2.53		
8	14	5.89	2.47		
9	16	6.26	2.44		
10	18	6.51	2.35		
11	20	6.72	2.25		

Calculation:-

$$1. I_L = \frac{V_L}{R_L} = \frac{1.65}{2} = 0.82 \text{ mA}$$

$$P_L = V_L \times I_L = 1.65 \times 0.82 = 1.36 \text{ mW} .$$

$$2. I_L = \frac{2.48}{3} = 0.826 \text{ mA}$$

$$P_L = 0.826 \times 2.48 = 2.05 \text{ mW}$$

$$3. I_L = \frac{2.90}{4} = 0.725 \text{ mA}$$


$$P_L = 0.725 \times 2.90 = 2.10 \text{ mW}$$

Teacher's Signature _____

Scatter

X-axis load
Y-axis load

100 200 300 400 500

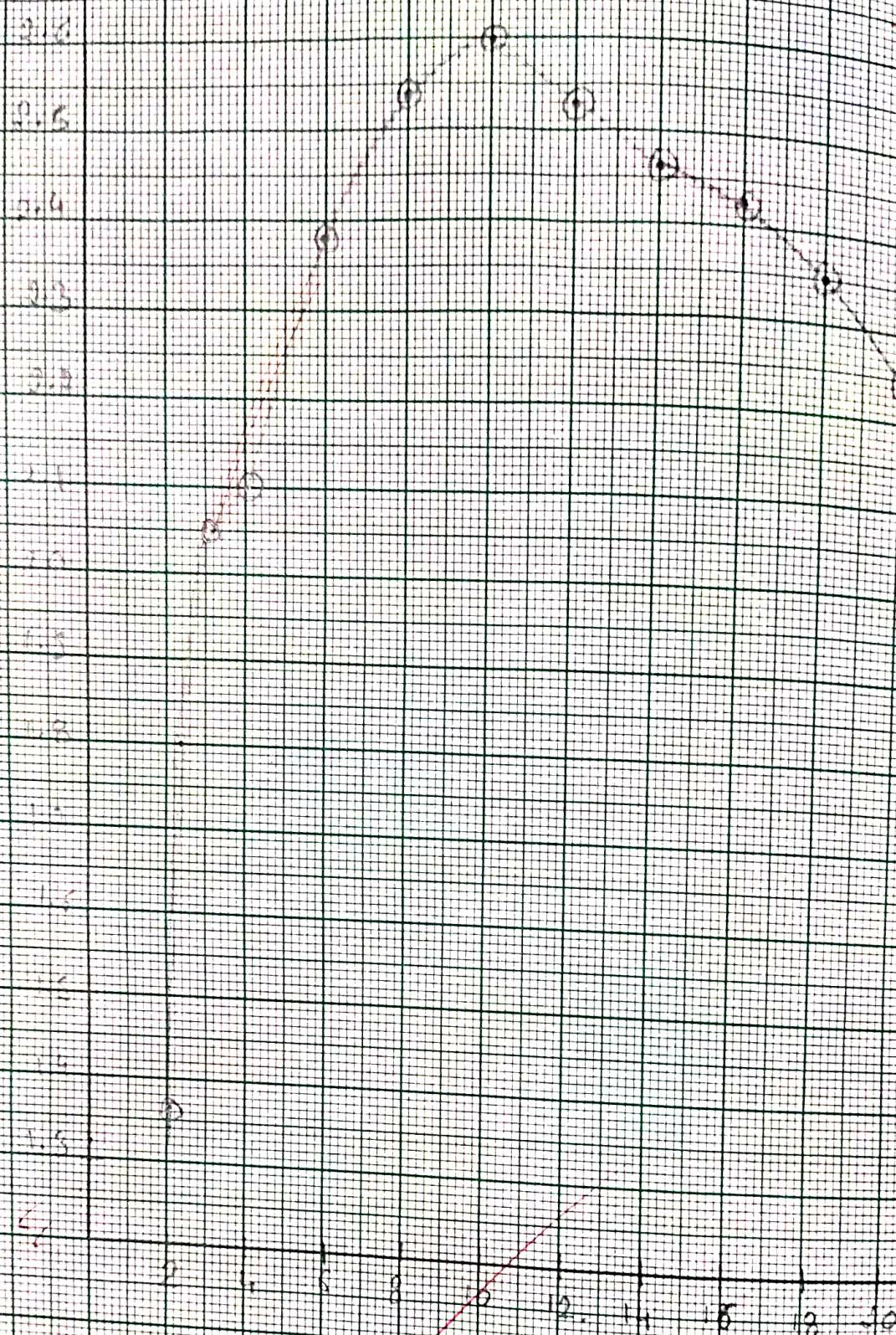

Relationship (load) (in Ω_{SL})

1 400 800

$$\begin{aligned} X \text{-axis} &= 0.1 \text{ k} \Omega \\ Y \text{-axis} &= 0.1 \text{ mW} \end{aligned}$$

4. $I_L = \frac{3.7}{6} = 0.616 \text{ mA}$

$$P_L = 0.563 \times 4.51 =$$

$$P_L = 0.616 \times 3.7 = 2.39 \text{ mW}$$

5. $I_L = \frac{4.51}{8} = 0.563 \text{ mA}$

$$P_L = 0.563 \times 4.51 = 2.54 \text{ mW}$$

6. $I_L = \frac{5.09}{10} = 0.50 \text{ mA}$

$$P_L = 0.506 \times 5.09 = 2.59 \text{ mW}$$

7. $I_L = \frac{5.53}{12} = 0.460 \text{ mA}$

$$P_L = 0.460 \times 5.53 = 2.53 \text{ mW}$$

8. $I_L = \frac{5.89}{14} = 0.420 \text{ mA}$

$$P_L = 0.420 \times 5.89 = 2.47 \text{ mW}$$

9. $I_L = \frac{6.26}{16} = 0.391 \text{ mA}$

$$P_L = 0.391 \times 6.26 = 2.44 \text{ mW}$$

10. $I_L = \frac{6.51}{18} = 0.361 \text{ mA.}$

$$P_L = 0.361 \times 6.51 = 2.35 \text{ mW.}$$

Teacher's Signature _____

11. $I_L = \frac{6.72}{20} = 0.336 \text{ mA}$


$$P_L = 0.336 \times 6.72 = 2.25 \text{ mW}$$

For theoretical max. Power transfer

$$P_{\max} = \frac{V^2}{4R_{\text{in}}} = \frac{(10)^2}{4 \times 10} = 2.5 \text{ mW}$$

Result

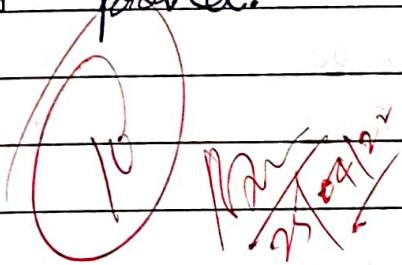Therefore verification of maximum power transfer theorem is proved.



Experiment - 6

Aim :

Study of Low Pass and High Pass Characteristics of RC Filter Circuits

- Study of transfer function and phase shift of a low pass RC filter network.
- Study the transfer function and phase shift of a high pass RC filter network.

Apparatus Required

Bread-Board, Digital Multimeter, Digital Oscilloscope, Resistors, Capacitors, Connecting wires, Testing probes, CRO probes, Function generator, etc.

Theory

1) Low Pass Filter

It is used to filter noise from a circuit. 'Noise' is a high frequency signal. When passed through a low pass filter most of the noise is removed and a clear sound is produced.

2) High Pass Filter


The filters are used in speakers for amplification. High Pass filter is used to remove unwanted sound near to the lower end of the available range.

Observation

Table 1: For low pass.

S. No.	$F(Hz)$	$V_{in}(V)$	$V_{out}(V)$	$A_v = \frac{V_{out}}{V_{in}}$
1	20	10	10.00	1
2	40	10	9.60	0.96
3	60	10	9.20	0.92
4	80	10	8.80	0.88
5	100	10	8.40	0.89
6	120	10	7.66	0.76
7	140	10	7.20	0.72
8	160	10	6.80	0.68
9	180	10	6.40	0.64
10	200	10	6.00	0.60
11	220	10	5.60	0.56
12	240	10	5.20	0.52
13	260	10	5.00	0.50
14	280	10	4.80	0.48
15	300	10	4.80	0.48

i) Low Pass

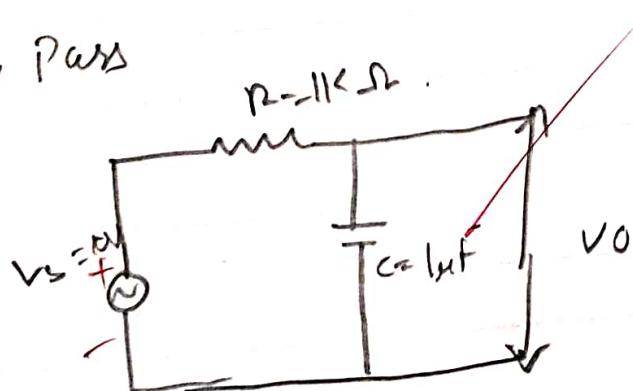

Formula Used:-

$$i) V_{in} = \left(R + \frac{1}{j\omega C} \right)$$

$$ii) V_o = \frac{J}{j\omega C}$$

$$iii) A_v = \frac{V_o}{V_{in}} = \frac{1}{1 + j\omega RC}$$

Observation

Value of low pass and high pass is shown in Table 1st and Table 2nd respectively.

Calculation

i) for Lower Pass:-

$$1) A_v = \frac{10}{10} = 1$$

$$2) A_v = \frac{9.60}{10} = 0.96$$

$$3) A_v = \frac{9.20}{10} = 0.92$$

$$4) A_v = \frac{8.80}{10} = 0.88$$

$$5) A_v = \frac{8.40}{10} = 0.84$$

$$6) A_v = \frac{7.60}{10} = 0.76$$

$$7) A_v = \frac{7.20}{10} = 0.72$$

$$8) A_v = \frac{6.80}{10} = 0.68$$

(ii) For High Pass

$$1) A_v = \frac{2.10}{10} = 0.21$$

$$2) A_v = \frac{3.10}{10} = 0.31$$

$$3) A_v = \frac{4.10}{10} = 0.41$$

$$4) A_v = \frac{4.80}{10} = 0.48$$

$$5) A_v = \frac{5.60}{10} = 0.56$$

$$6) A_v = \frac{6.40}{10} = 0.64$$

$$7) A_v = \frac{6.80}{10} = 0.68$$


$$8) A_v = \frac{7.20}{10} = 0.72$$

Teacher's Signature _____

Table 2nd : For high pass

S. No.	$F(Hz)$	$V_{in} (V)$	$V_{out} (V)$	$A_v = \frac{V_{out}}{V_{in}}$
1	20	10	2.10	0.21
2	40	10	3.10	0.31
3	60	10	4.12	0.41
4	80	10	4.80	0.48
5	100	10	5.60	0.56
6	120	10	6.40	0.64
7	140	10	6.80	0.68
8	160	10	7.20	0.72
9	180	10	7.60	0.76
10	200	10	8.00	0.80
11	220	10	8.20	0.82
12	240	10	8.40	0.84
13	260	10	8.60	0.86
14	280	10	8.80	0.88
15	300	10	8.80	0.88

2) High Pass Filter

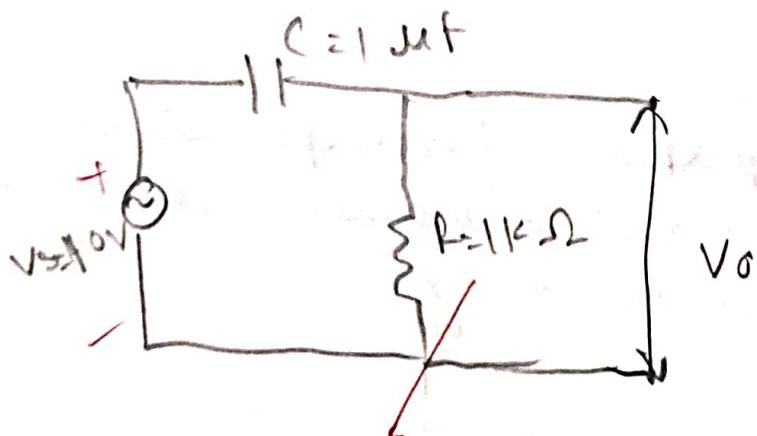

$$9) A_v = \frac{6.90}{10} = 0.69$$

$$g) A_v = \frac{7.60}{10} = 0.76$$

$$10) A_v = \frac{6.00}{10} = 0.60$$

$$10) A_v = \frac{8.00}{10} = 0.80$$

$$11) A_v = \frac{5.60}{10} = 0.56$$

$$11) A_v = \frac{8.20}{10} = 0.82$$

$$11) A_v = \frac{5.20}{10} = 0.52$$

$$12) A_v = \frac{8.40}{10} = 0.84$$

$$13) A_v = \frac{5.00}{10} = 0.50$$

$$13) A_v = \frac{8.60}{10} = 0.86$$

$$14) A_v = \frac{4.80}{10} = 0.48$$

$$14) A_v = \frac{8.80}{10} = 0.88$$

$$15) A_v = \frac{4.80}{10} = \cancel{0.48}$$

$$15) A_v = \frac{8.80}{10} = 0.88$$

iii Cut-off frequency

$$\omega = 2\pi f$$

$$f = 0.$$

$$f_c = \frac{1}{2\pi R C} = \frac{1}{2\pi \times 1.0 \times 10^2 \times 1.0 \times 10^{-6}}$$

$$f_c = 159.15 \text{ Hz}$$

$$f_2 = 160 \text{ Hz}$$

when,

$$\omega \rightarrow 0$$

$H(j\omega)$ is zero

Scat

$$Y = 0.021 + 0.01 = 0.03$$

Y

1.1

↑

1.0

0.5

0.3

0.2

0.6

0.5

0.4

0.3

0.2

0.1

20 40 60 80

100 120 140

160 180 200

220 240 260

280 300 320

340 360 380

400 420 440

460 480 500

520 540 560

580 600 620

640 660 680

700 720 740

760 780 800

820 840 860

880 900 920

940 960 980

1000 1020 1040

1060 1080 1100

1120 1140 1160

1180 1200 1220

1240 1260 1280

1300 1320 1340

1360 1380 1400

1420 1440 1460

1480 1500 1520

1540 1560 1580

1620 1640 1660

1700 1720 1740

1760 1780 1800

1820 1840 1860

1900 1920 1940

1960 1980 2000

2020 2040 2060

2080 2100 2120

2140 2160 2180

2200 2220 2240

2260 2280 2300

2320 2340 2360

2380 2400 2420

2440 2460 2480

2500 2520 2540

2560 2580 2600

2620 2640 2660

2680 2700 2720

2740 2760 2780

2800 2820 2840

2860 2880 2900

2920 2940 2960

2980 3000 3020

3040 3060 3080

3100 3120 3140

3160 3180 3200

3220 3240 3260

3280 3300 3320

3340 3360 3380

3400 3420 3440

3480 3500 3520

3560 3580 3600

3620 3640 3660

3700 3720 3740

3760 3780 3800

3820 3840 3860

3900 3920 3940

3960 3980 4000

4020 4040 4060

4100 4120 4140

4160 4180 4200

4220 4240 4260

4300 4320 4340

4360 4380 4400

4420 4440 4460

4500 4520 4540

4560 4580 4600

4620 4640 4660

4700 4720 4740

4760 4780 4800

4820 4840 4860

4900 4920 4940

4960 4980 5000

5020 5040 5060

5100 5120 5140

5160 5180 5200

5220 5240 5260

5300 5320 5340

5360 5380 5400

5420 5440 5460

5500 5520 5540

5560 5580 5600

5620 5640 5660

5700 5720 5740

5760 5780 5800

5820 5840 5860

5900 5920 5940

5960 5980 6000

6020 6040 6060

6100 6120 6140

6160 6180 6200

6220 6240 6260

6300 6320 6340

6360 6380 6400

6420 6440 6460

6500 6520 6540

6560 6580 6600

6620 6640 6660

6700 6720 6740

6760 6780 6800

6820 6840 6860

6900 6920 6940

6960 6980 7000

7020 7040 7060

7100 7120 7140

7160 7180 7200

7220 7240 7260

7300 7320 7340

7360 7380 7400

7420 7440 7460

7500 7520 7540

7560 7580 7600

7620 7640 7660

7700 7720 7740

7760 7780 7800

7820 7840 7860

7900 7920 7940

7960 7980 8000

8020 8040 8060

8100 8120 8140

8160 8180 8200

8220 8240 8260

8300 8320 8340

8360 8380 8400

8420 8440 8460

8500 8520 8540

8560 8580 8600

8620 8640 8660

8700 8720 8740

8760 8780 8800

8820 8840 8860

8900 8920 8940

8960 9000 9040

9020 9040 9060

9100 9120 9140

9160 9180 9200

9220 9240 9260

9300 9320 9340

9360 9380 9400

9420 9440 9460

9500 9520 9540

9560 9580 9600

9620 9640 9660

9700 9720 9740

9760 9780 9800

9820 9840 9860

9900 9920 9940

9960 10000 10040

for

$$\omega = \omega_0$$

$$H(j\omega_c) = \frac{1}{\sqrt{2}}$$

$$P \rightarrow 0$$

so,

f_v is max


~~$$\text{for } F = F_3, A_v = \frac{1}{\sqrt{2}} = 0.702 = 0.71 \text{ approx.}$$~~

Result

Here the high pass filter & low pass filter has been successfully verified.

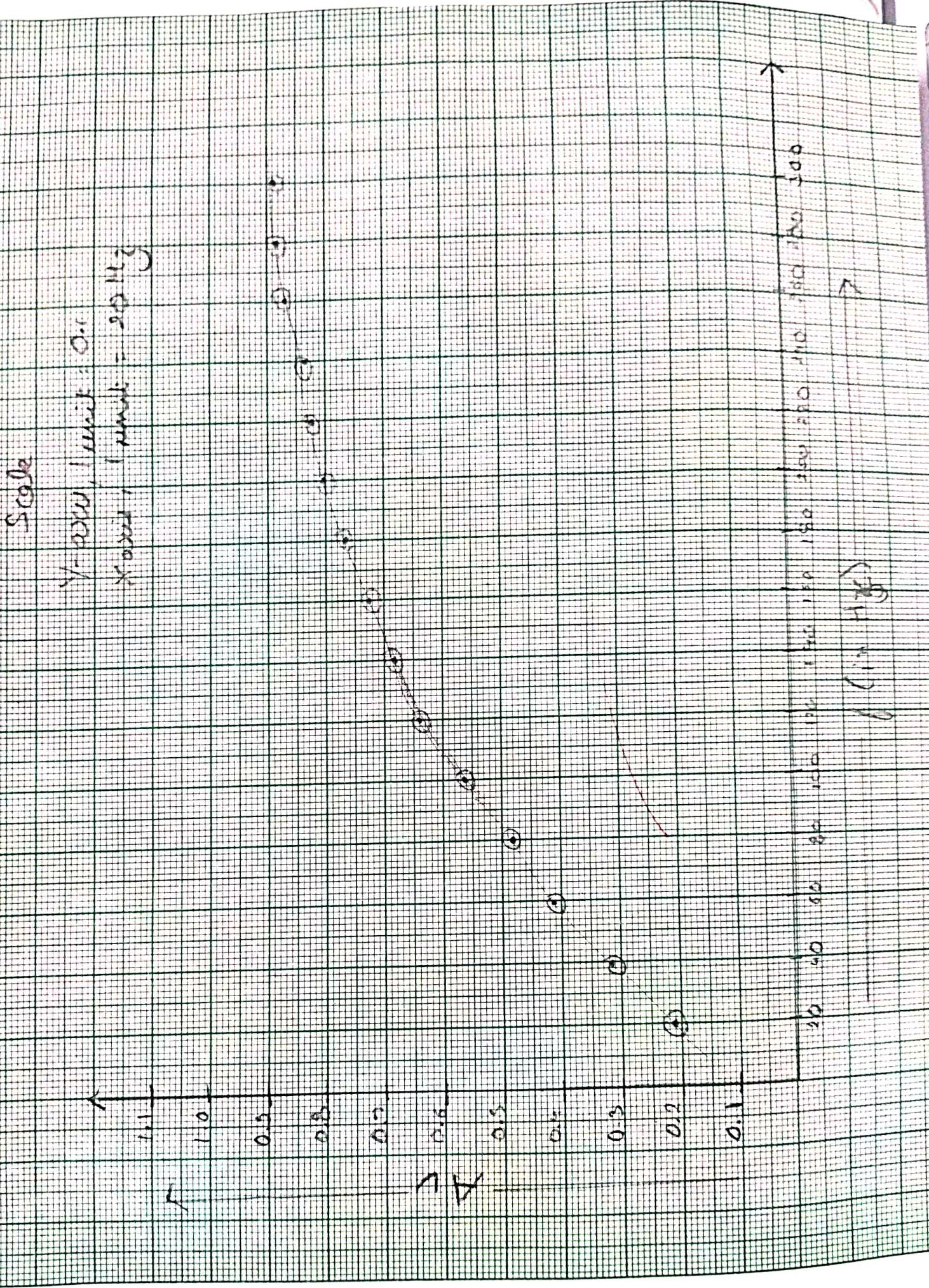(10)

~~$$\frac{1}{2\pi} \cdot \frac{1}{(0.3)^2}$$~~




Experiment - 7

Aim: To study and measurement of voltage current ($V-I$) characteristic of a p-n junction diode (Ge or Si)

Apparatus Required: Variable DC power supply (0-30V), Breadboard, Multimeters (two Nos.), pn junction diode, resistors of different values, connecting wires and crocodile clips, Resistors of different values: $100\ \Omega$, $1\ K\Omega$, $10\ K\Omega$, $100\ K\Omega$ and $1\ M\Omega$


Theory - A pn junction diode is active electronics component made of semiconductor material such as silicon (Si). The basic feature of the diode is that it conducts significantly when forward biased, beyond a certain critical voltage called "diode-cut-in voltage". Forward biasing refers to the p-side connected to positive and n-side connected to negative terminal of battery. For p-n junction diode made in silicon, the value of cut-in voltage is about 0.7 V. For diodes made in Germanium (Ge) semiconductor material, the corresponding value is of the order of 0.3 V. In the reverse bias conditions (n-side connected to positive terminal and p-side to negative terminal of battery), negligible current flows through the diode till the voltage reaches the breakdown value.

Circuit Diagram.

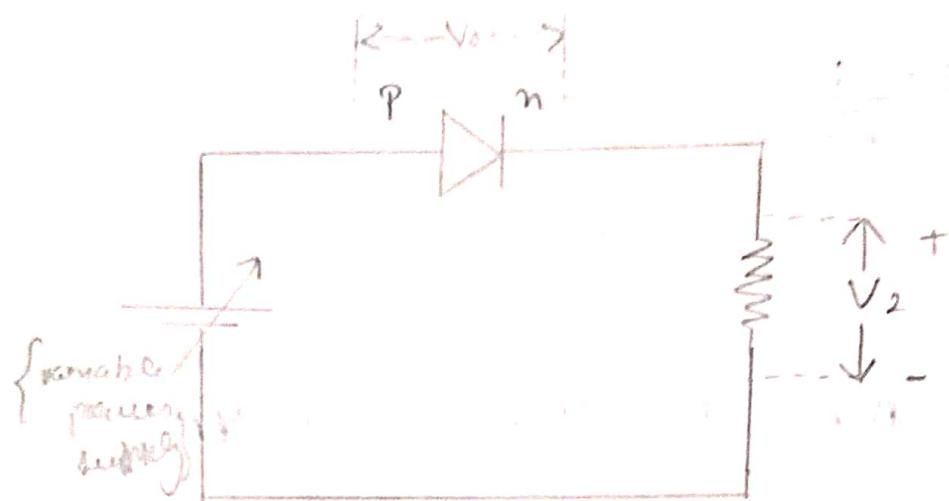


Forward bias

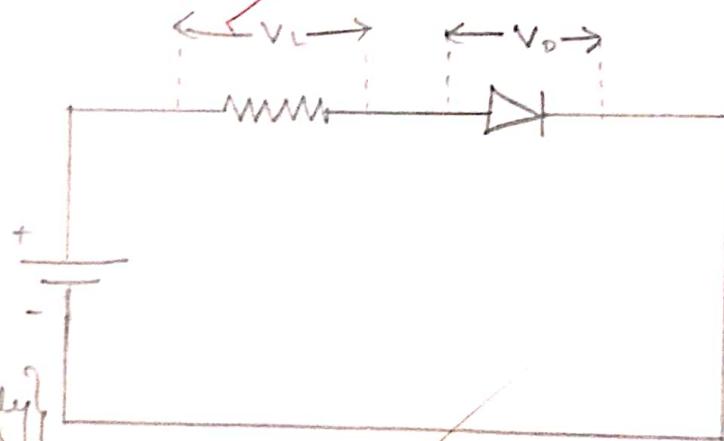~~Diagram is a zener diode with variable power supply across it. It is forward biased.~~



Reverse bias

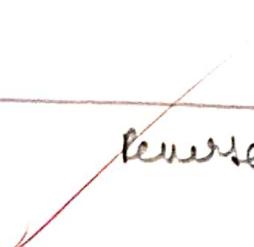

	V_i (in V)	V_d (in V)	V_L (in V)	$I_L = \frac{V_L}{R_L}$ (mA) { $R_L = 1k\Omega$ }
0	0	0	0	0.0
0.2	0.159	0.003	0.009	0.009
0.4	0.390	0.009	0.009	0.009
0.6	0.488	0.111	0.111	0.111
0.8	0.528	0.27	0.27	0.27
1.0	0.553	0.495	0.495	0.495
1.2	0.576	0.627	0.627	0.627
1.4	0.587	0.816	0.816	0.816
1.6	0.592	1.004	1.004	1.004
1.8	0.6	1.199	1.199	1.199
2.0	0.608	1.390	1.390	1.390
2.6	0.620	1.778	1.778	1.778
2.8	0.630	2.168	2.168	2.168
3.0	0.634	2.366	2.366	2.366
3.5	0.644	2.952	2.952	2.952
4.0	0.649	3.345	3.345	3.345
5.0	0.661	4.340	4.340	4.340

Calculationfor forward bias current

$$I_L = \frac{V_L}{R_L} \text{ (mA)}$$

where $R_L = 1k\Omega$

hence $I_L = \frac{V_L}{1000\Omega}$

$$I_L = V_L \text{ (mA)}$$

for each case

Topic : _____

Date : _____

Scallop graph

Y-axis 1 unit = 0.2 Amperes

X-axis 1 unit = 0.5 Volts

Axis

I_L (Amp)

4.2

4.0

3.8

3.6

3.4

3.2

3.0

2.8

2.6

2.4

2.2

2.0

1.8

1.6

1.4

1.2

1.0

0.8

0.6

0.4

0.2

0.05 0.10 0.15 0.20 0.25 0.30 0.35 0.40 0.45 0.50 0.55 0.60 0.65 0.70

V_d (Volts)

←

Axis →



Result

The data on IV measurement is plotted on a graph sheet to compare the diode behaviour in forward bias condition.

~~Plot of V_D vs I_D~~
10 100 1000

Experiment - 8

Aim: (a) To study V-I characteristic of zener diode
(b) To study zener diode as a voltage regulator.



Apparatus Used: dc power supply (0-30V), zener diode, resistor, multimeter, bread board, connecting wire.

Theory: A p-n junction diode normally does not conduct with reverse bias. But if the reverse bias is increased at a particular voltage it starts conducting heavily. This voltage is called breakdown voltage. High current through the diode can permanently damage it. To avoid high current, with connected resistor in series with it. Once the diode starts conducting, it maintains almost constant current across its terminal whatever may be current through it. It has very low dynamic resistance.

A zener diode is p-n junction diode especially made to work in breakdown region. It is used as a voltage regulator.

Dynamic Resistance
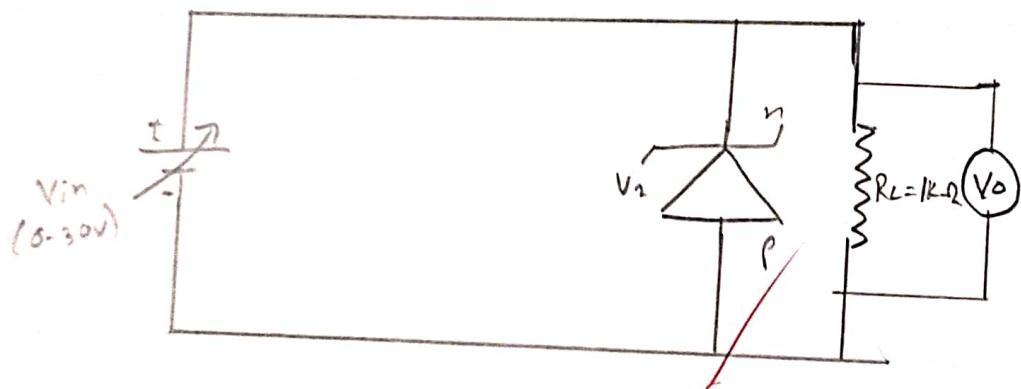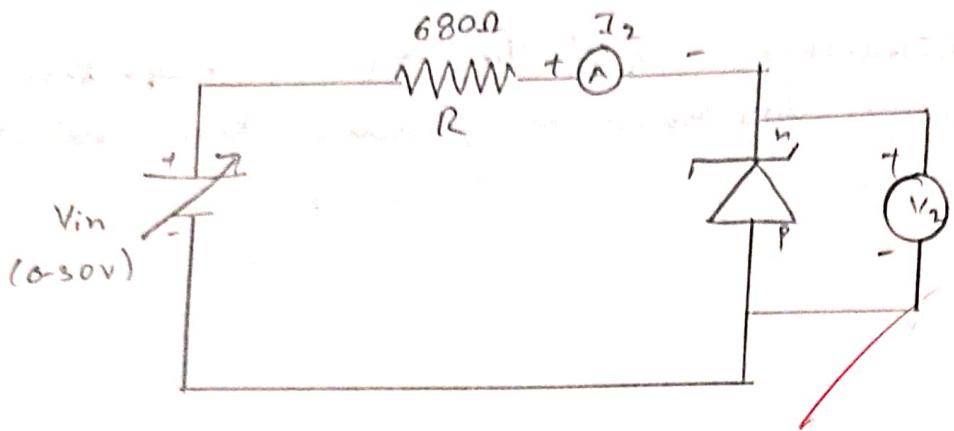
$$r_d = \frac{\Delta V_z}{\Delta I_z} = \frac{AB}{CD}$$



Observation Table 1

SNo	$V_{in}(V)$	$V_2(V)$	$I_L = V_2 / R \text{ (mA)}$
1	0	0	0
2	1	1.092	0
3	2	2.150	0
4	3	3.12	0
5	4	4.16	0
6	5	5.15	0
7	6	6.13	0
8	7	7.18	0
9	8	8.15	0
10	9	9.13	0
11	10	10.13	0
12	11	11.18	0
13	12	12.15	0.001
14	13	13.16	0.001
15	14	14.12	0.001
16	15	14.94	0.410
17	16	15.03	1.601
18	17	15.10	2.8
19	18	15.24	4.0
20	19	15.34	5.3
21	20	15.42	6.6
22	21	15.50	7.8
23	22	15.66	9.0
24	23	15.82	10.4
25	24	15.93	11.7
26	25	16.13	12.9

Scale

Lumel on \rightarrow

X-axis $\rightarrow 1V$

Y-axis $\rightarrow 1mA$

V_Z (V)

X-axis

-15 -14 -13 -12 -11 -10 -9 -8 -7 -6 -5 -4 -3 -2



Y-axis

10

11

12

13

14

15

Observation Table 2.

No.	$V_{in} (V)$	$V_o (V)$
01.	1	0.682
02.	2	1.284
03.	3	1.878
04.	4	2.478
05.	5	3.06
06.	6	3.61
07.	7	4.04
08.	8	4.32
09.	9	4.49
10.	10	4.61
11.	11	4.67
12.	12	4.72.
13.	13	4.76
14.	14	4.80
15.	15	4.84
16.	16	4.87
17.	17	4.90
18.	18	4.92.
19.	19	4.94
20.	20	4.95.

Result

- a) The study of V-I characteristics have been successfully performed.
- b) The study of zener diode as a voltage regulator has been successfully performed.
- ~~Q/A Ch 21 S 21~~

Date:

Scale: Direct

V - air : 1 V
V - ave : 1 V

V_{ave}

1.0

0.5

0.3

0.2

0.1

0.05

0.02

0.01


0.005

0.002

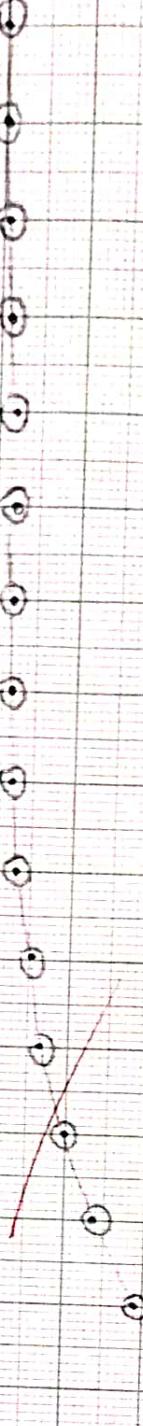0.001

$y_{in} (cm)$

21
20
18
16
15
14
13
12
11
10
9
8
7
6
5
4
3
2
1
0



Experiment - 9

Aim: To design and study of half wave rectifier (without and with capacitance) on bread board and observe the input and output waveform. Also calculate the output voltage (V_{rms}), DC output voltage (V_{dc}), DC current (I_{dc}) and ripple factor.

Apparatus Used: Function generator, DSO, diode, resistors, multimeter, bread board, connecting wires.



Theory: Half wave rectifier is primarily used to convert a given AC signal into a DC signal. Power transmitted from power stations is an AC signal (220 V / 50 Hz) whereas most of the home appliances or other electrical equipment we use in our day-to-day life require DC power. The method by which we convert a given AC signal into a DC signal is called 'rectification'. In this experiment, one such basic circuit used for rectification is built. The DC output current.

Formula Used

$$1. \text{ AC input voltage } (V_{rms}) = \frac{V_m}{2}$$



$$2. \text{ DC output voltage } (V_{dc}) = \frac{V_m}{\pi}$$
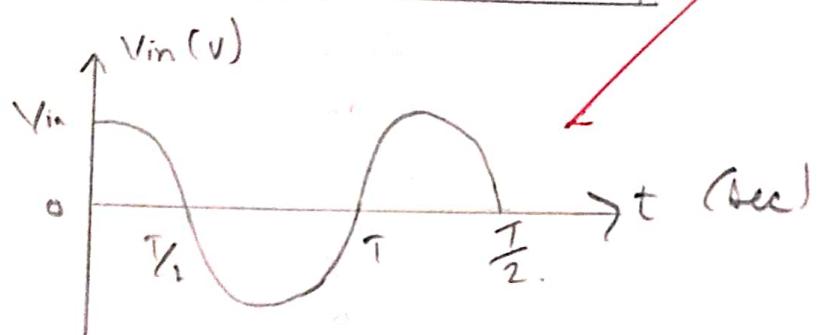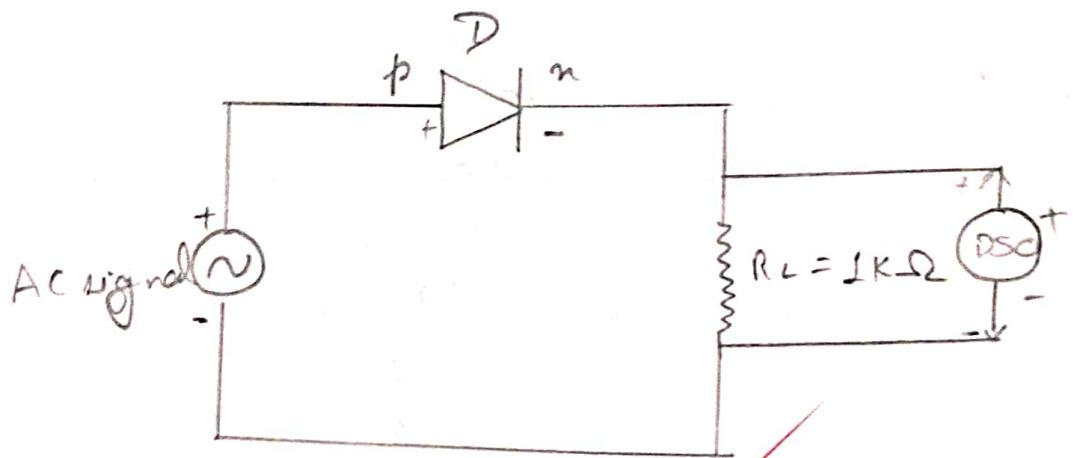
$$3. \text{ DC current } (I_{dc}) = \frac{I_m}{\pi}$$



During the half cycle

$$0 \rightarrow \frac{T}{2}$$

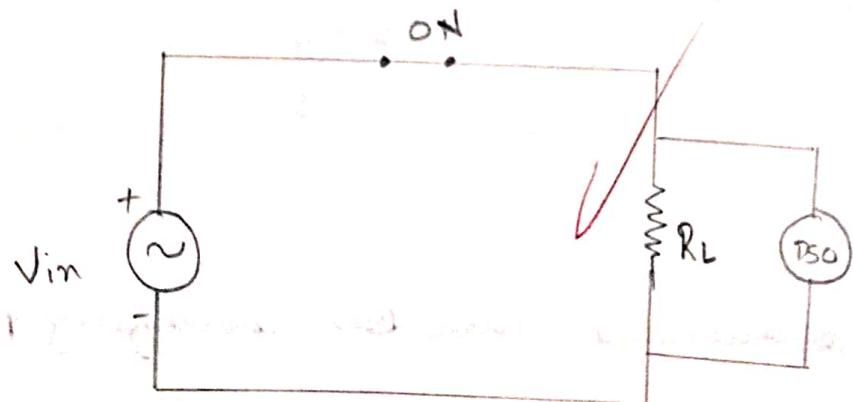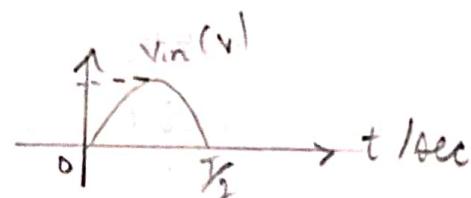

Equivalent circuit during the half cycle

Expt. No.


4) Ripple factor $\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$

$$I_{rms} = \frac{I_m}{2}$$

$$\gamma = \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1}$$

Observation

Output waveform without capacitor.

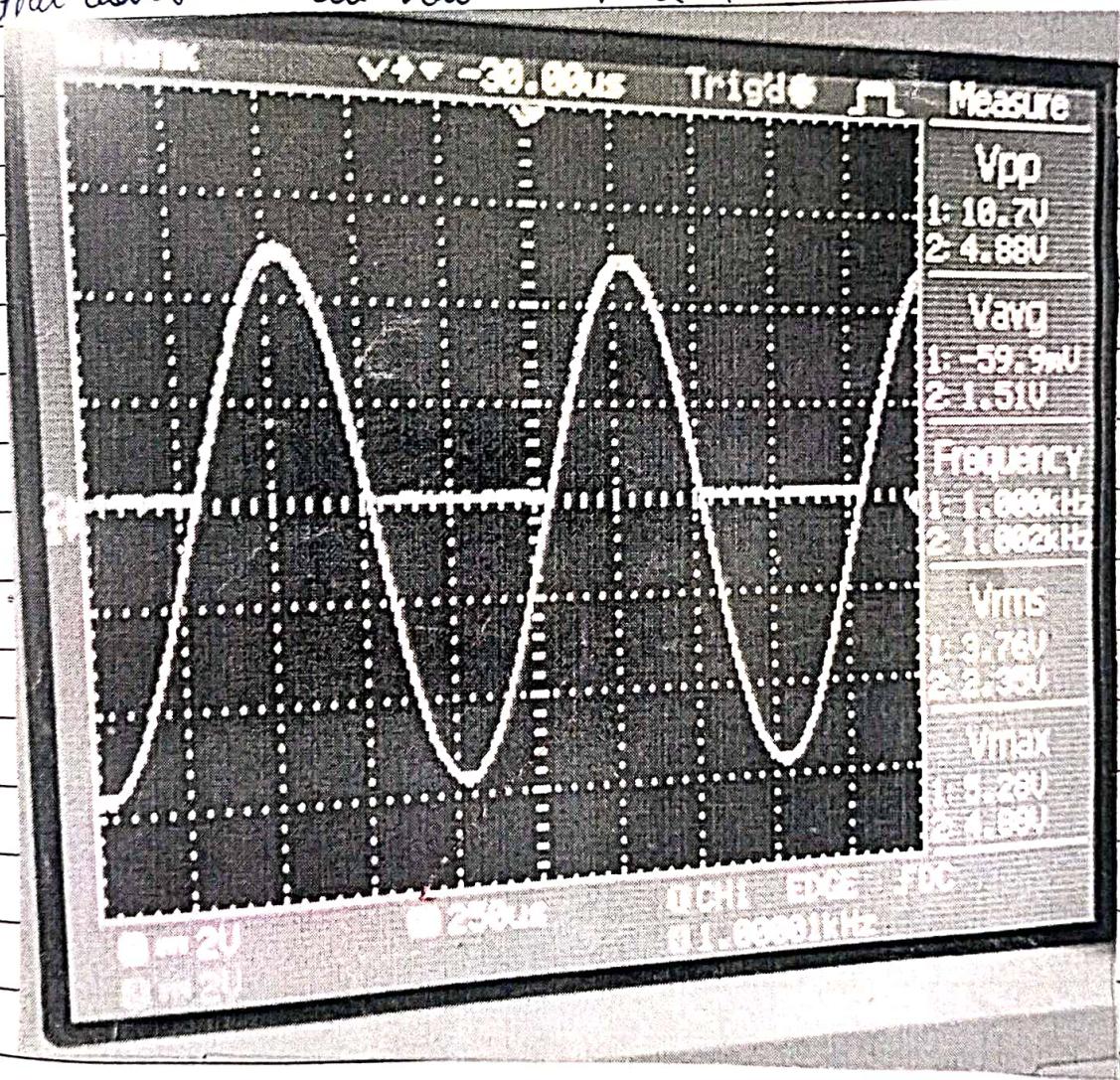


Calculation

Without capacitor


$$V_{pp} = 8.11 \times 10 \text{ mV} = 10.7$$

$$V_m = \frac{V_{pp}}{2} = \frac{8.11 \times 10}{2} = 5.35 \text{ V}$$




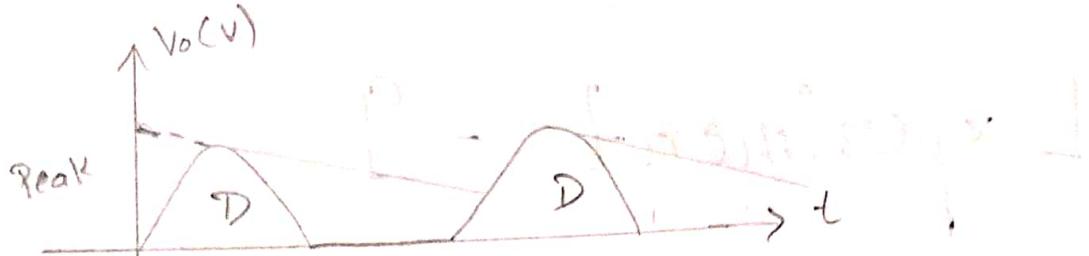
$$R = 1 \text{ k}\Omega = 1 \times 10^3 \Omega$$



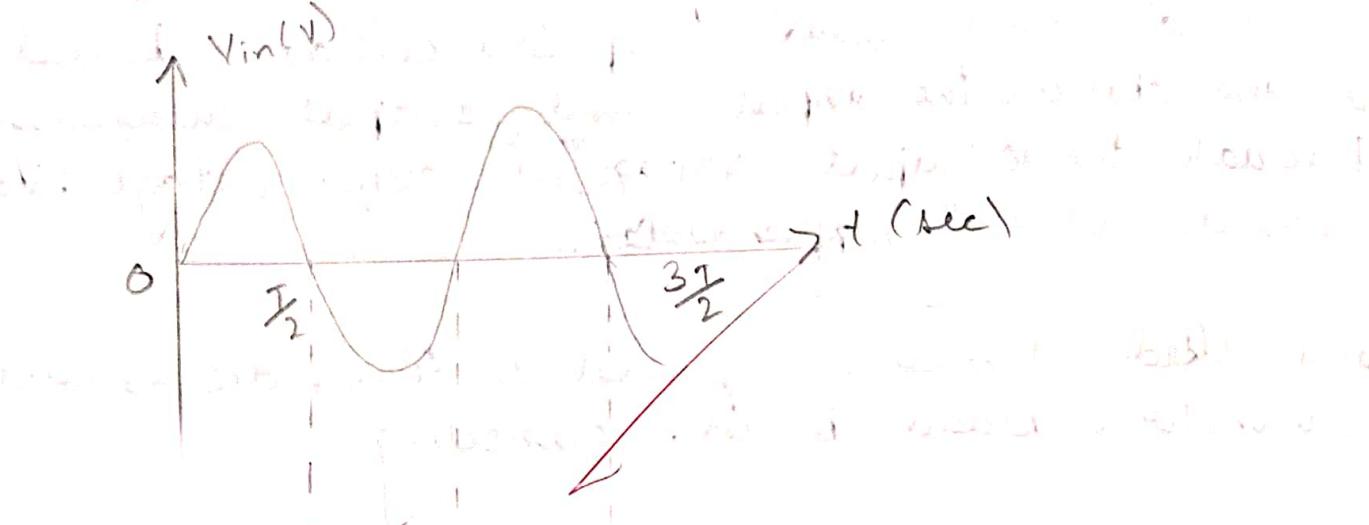Half cycle voltage across load & across tank capacitor



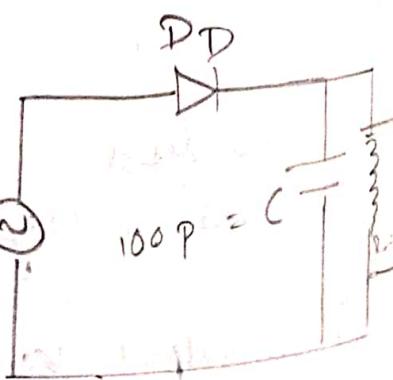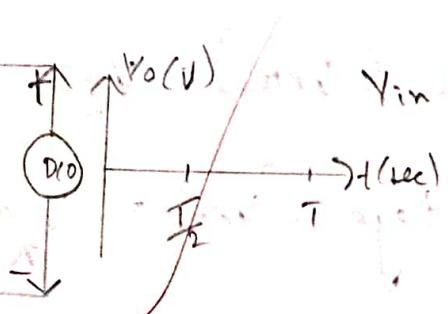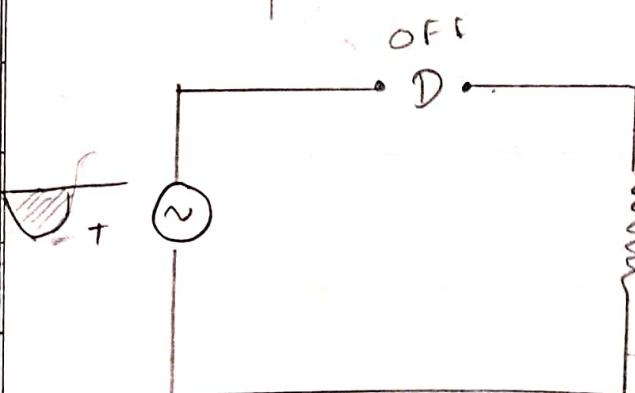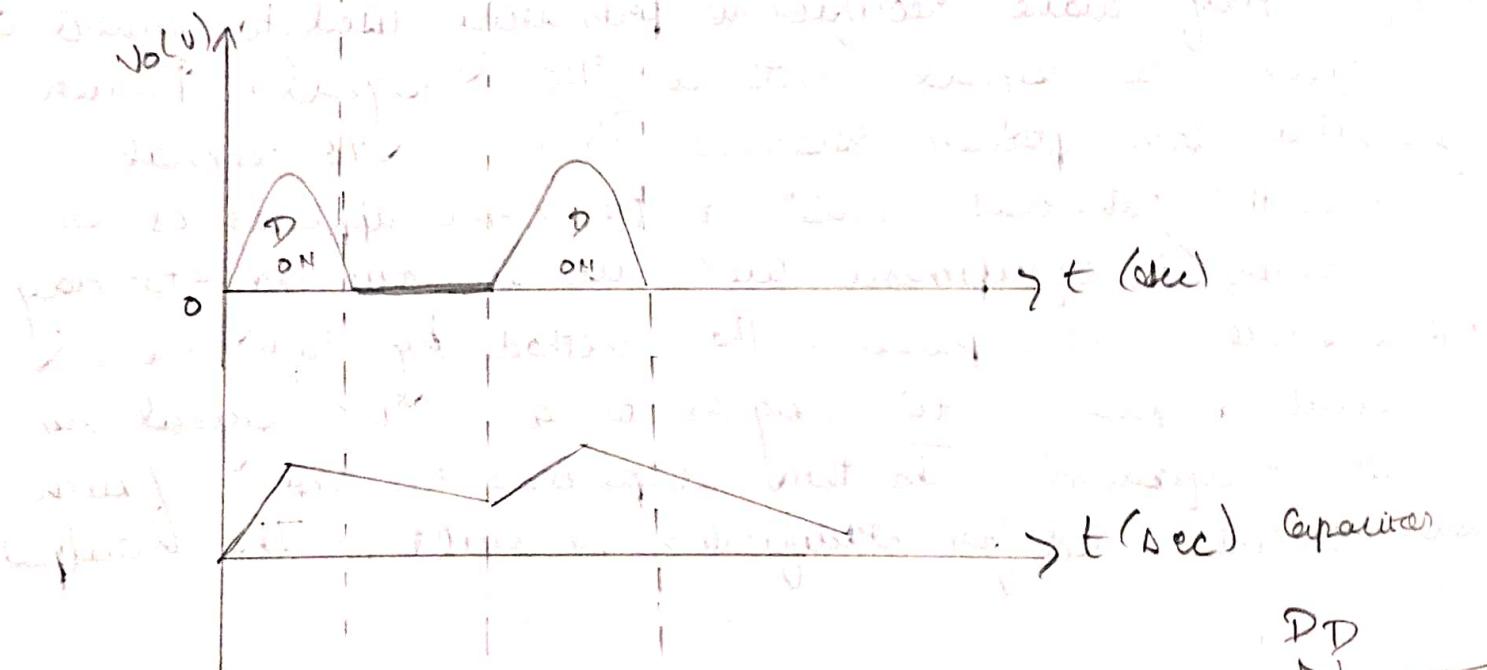Half cycle voltage across load & across tank capacitor



1) AC input voltage (V_{RMS}) = $\frac{V_m}{\sqrt{2}} = \frac{5.35}{\sqrt{2}} = 2.67$ volts.

2) DC output voltage (V_{dc}) = $\frac{V_m}{\pi} = \frac{5.35}{\pi} = 1.703$

3) $I_m = \frac{V_m}{R} = \frac{5.35}{1 \times 10^3} = 5.35 \times 10^{-3} A$

DC current (I_{dc}) = $\frac{V_m}{\pi} = \frac{1.70 \times 10^{-3}}{\pi} A$

4) Ripple factor $\eta = \sqrt{\left(\frac{T_m/2}{I_m/\pi}\right)^2 - 1} \approx$

$$= \sqrt{\left(\frac{(5.35 \times 10^{-3})}{2}\right)^2 - 1}$$

$$\frac{1.70 \times 10^{-3}}{3.14 \times 10^{-3}}$$

$$= \sqrt{\left(\frac{0.002}{0.541}\right)^2 - 1} = \sqrt{\left(\frac{267}{0.54}\right)^2 - 1}$$

$$= \sqrt{(0.003)^2 - 1} = 4.83$$

$$= 0.957$$

With capacitor.

$V_{pp} = 2152 \cdot 7.52 V$ $R = 1 k\Omega = 1 \times 10^3 \Omega$


$V_m = \frac{V_{pp}}{2} = \frac{7.52}{2} = 3.76 V$

1) AC input voltage (V_{RMS}) = $\frac{V_m}{\sqrt{2}} = \frac{3.76}{\sqrt{2}} = 1.88 V$

2) DC output voltage (V_{dc}) = $\frac{V_m}{\pi} = \frac{3.76}{\pi} = 1.197 V$

3) $I_m = \frac{V_m}{R} = \frac{3.76}{1 \times 10^3} = 3.76 \times 10^{-3} A$

Teacher's Signature _____

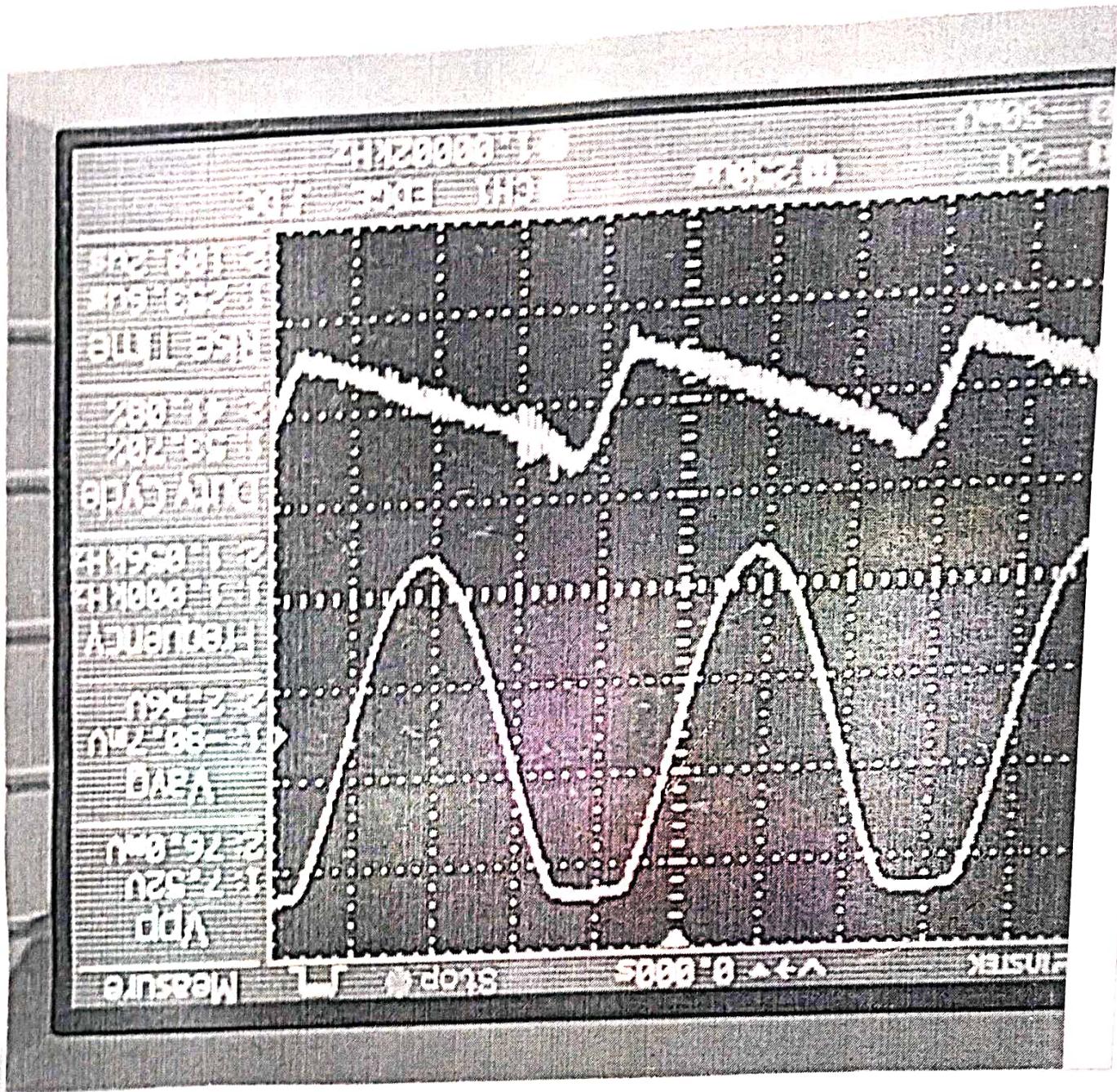

$$\text{DC current } (I_{dc}) = \frac{I_m}{\pi} = \frac{3.76 \times 10^{-3}}{3.14} = 1.19 \times 10^{-3} \text{ A}$$

$$\text{Ripple factor } \gamma = \sqrt{\frac{(I_m/2)^2 - 1}{(I_m/\pi)^2}}$$

$$= \sqrt{\left(\frac{1.88 \times 10^{-3}}{1.19 \times 10^{-3}}\right)^2 - 1}$$

$$= 1.211$$

Result

The experiment was successfully conducted.

$$\gamma (\text{without capacitor}) = 4.83$$

$$\gamma (\text{with capacitor}) = 1.211$$

(S)

~~For 23/5/2017~~



Experiment - 10

Aim - To design a bridge rectifier circuit (without and with capacitors) and also plot the output waveform. Calculate peak values, rms value and ripple factor.

Apparatus Used : Diode, capacitor form, resistance, step down transformer, DSO, bread board, connecting wire

During +ve half cycle $0 \rightarrow \frac{T}{2}$





Theory without capacitor

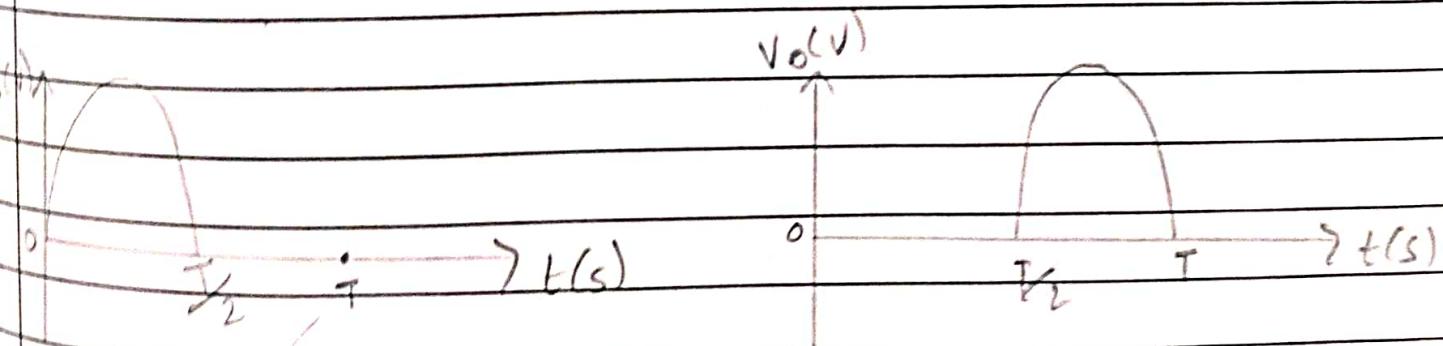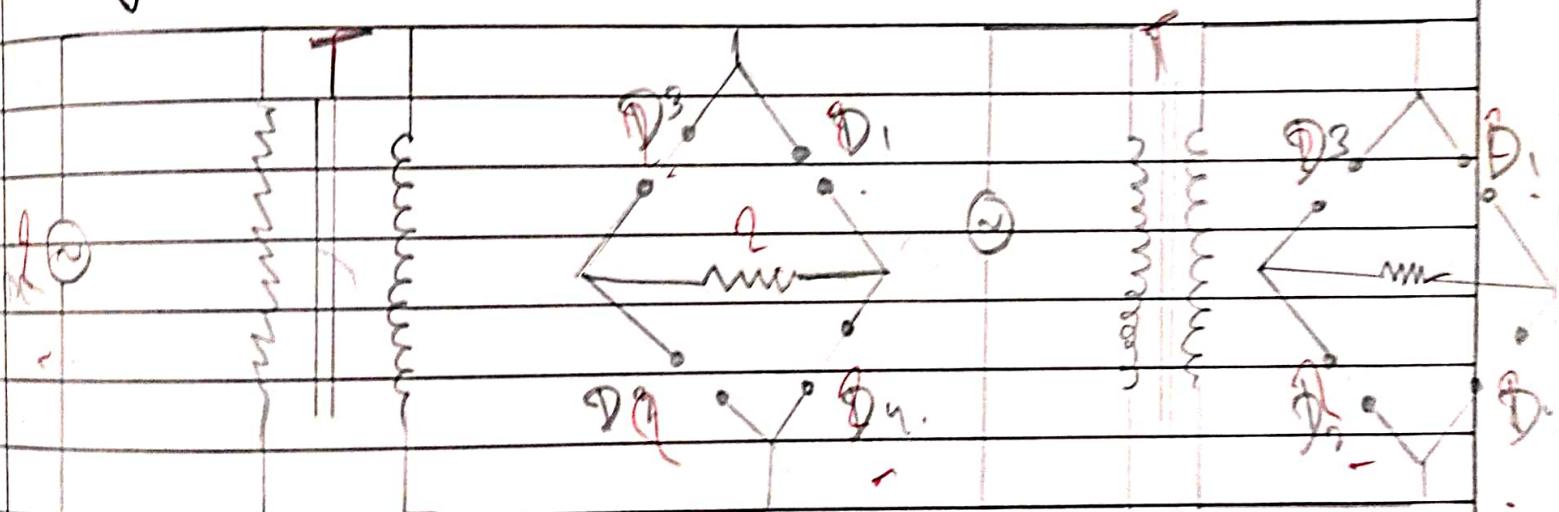

D₁, D₂ → ON

D₃, D₄ → ON



Teacher's Signature _____

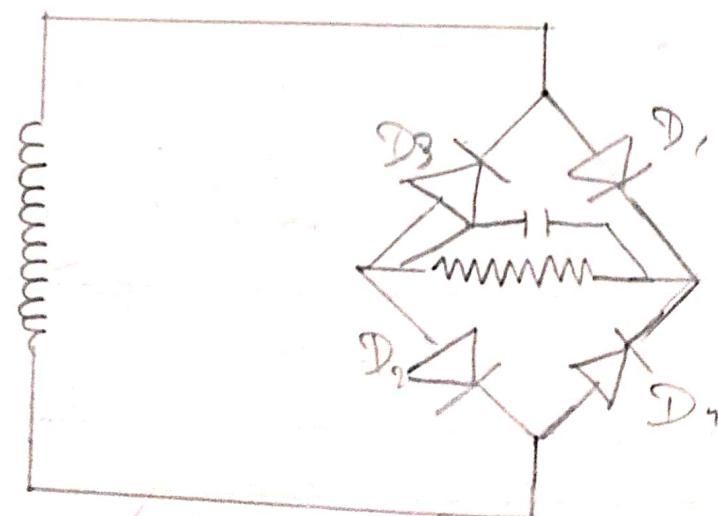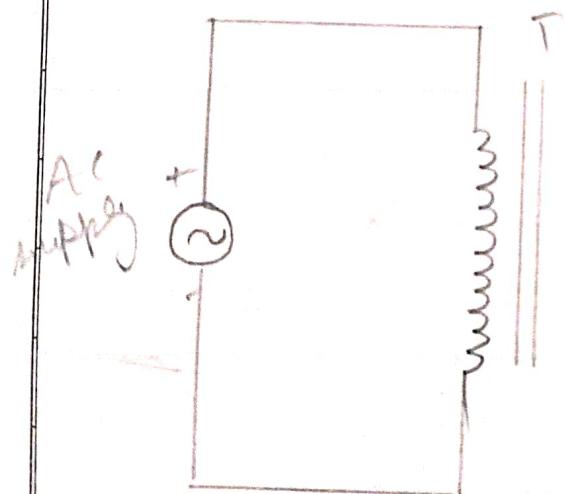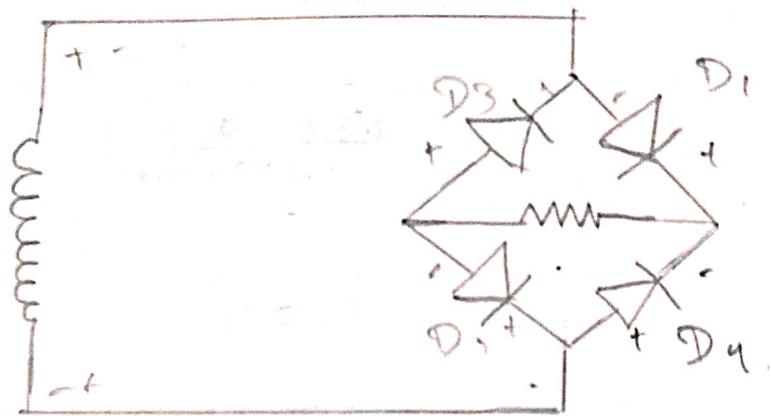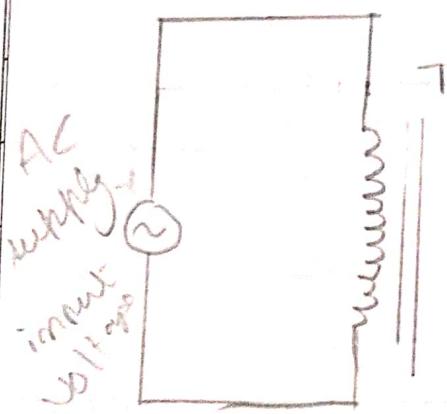

~~Without capacitor.~~

Expected waveform.

Input waveform:

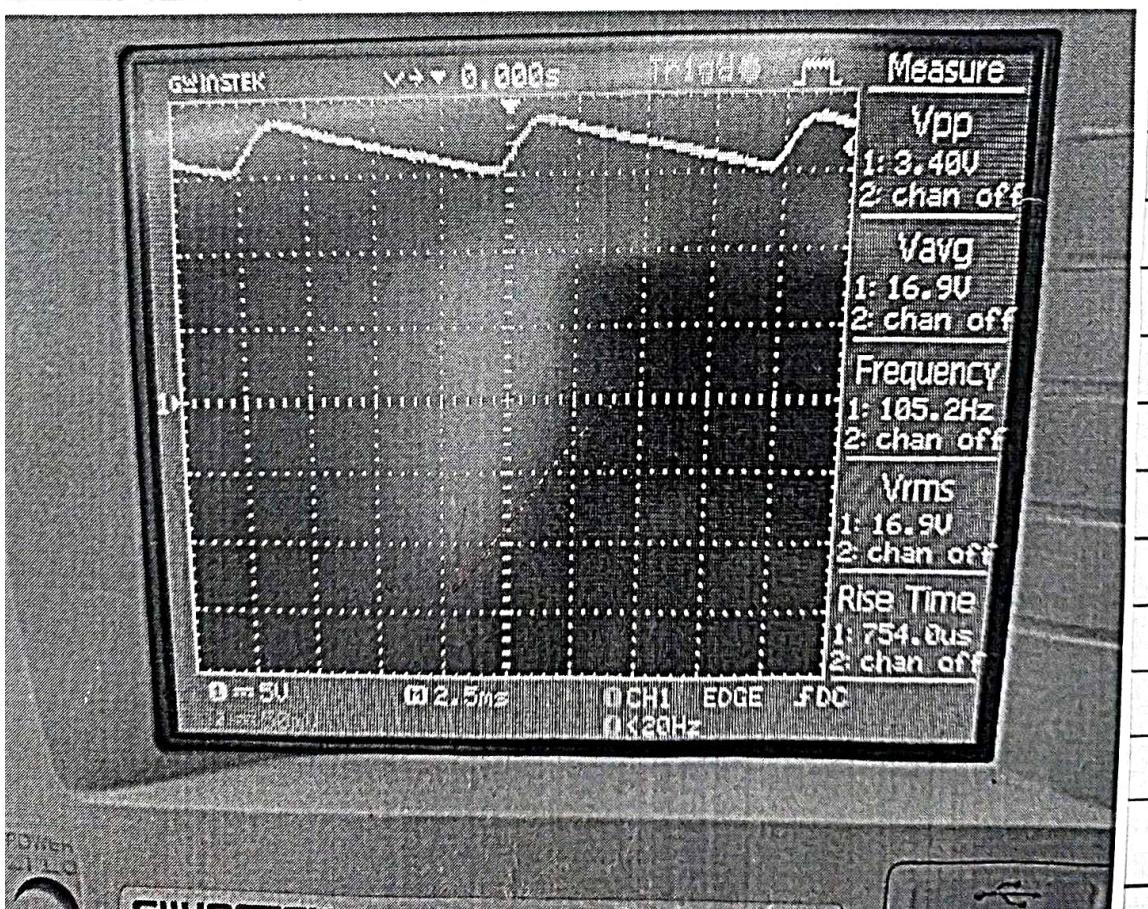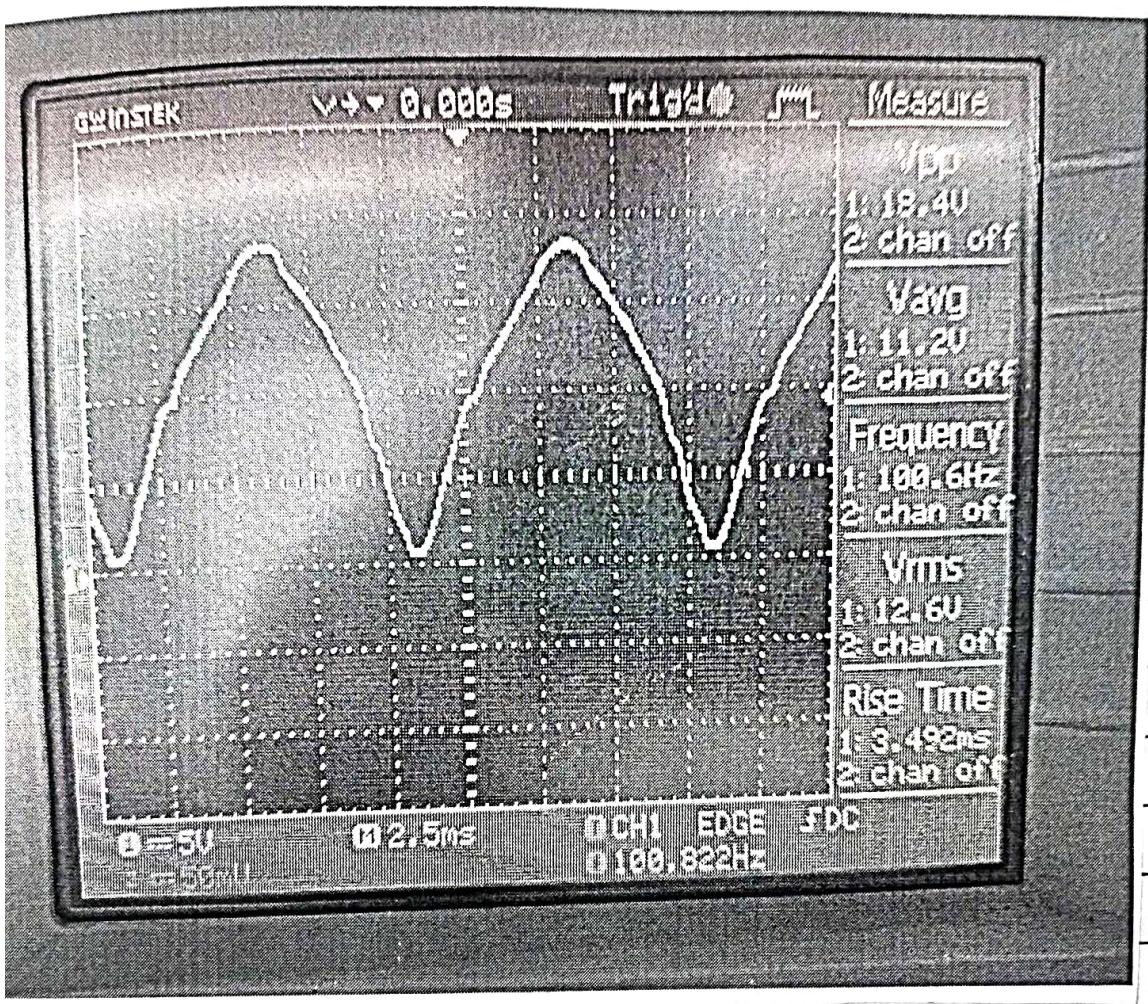

Observation :-

Without capacitor.

V_{pp} (V)	V_{avg} (V)	V_{rms} (V)	freq (Hz)	Ripple factor (%)
18.4	11.2	12.6	100.6	0.515

$$\text{Ripple factor} = \sqrt{\frac{(V_{rms})^2 - 1}{(V_{avg})^2}} = \sqrt{\frac{(12.6)^2 - 1}{(11.2)^2}} = 0.515$$

With capacitor.

V_{pp} (V)	V_{avg} (V)	V_{rms} (V)	freq (Hz)	Ripple factor (%)
3.40	16.15	16.3	105.2	1.

$$\text{Ripple factor} = \sqrt{\frac{(V_{rms})^2 - 1}{(V_{avg})^2}} = \sqrt{\frac{(16.3)^2 - 1}{(16.15)^2}} = 0.1$$

Result

The experiment was successfully conducted R.F. of without rectifier and with rectifier is 0

(8)

Mr. S. S. S.


Teacher's Signature _____

Experiment - 11


Aim - Design and study clipper circuit.

Apparatus Used = Function generator, DSO, dc power supply, resistance, bread board, probe and connecting wire.


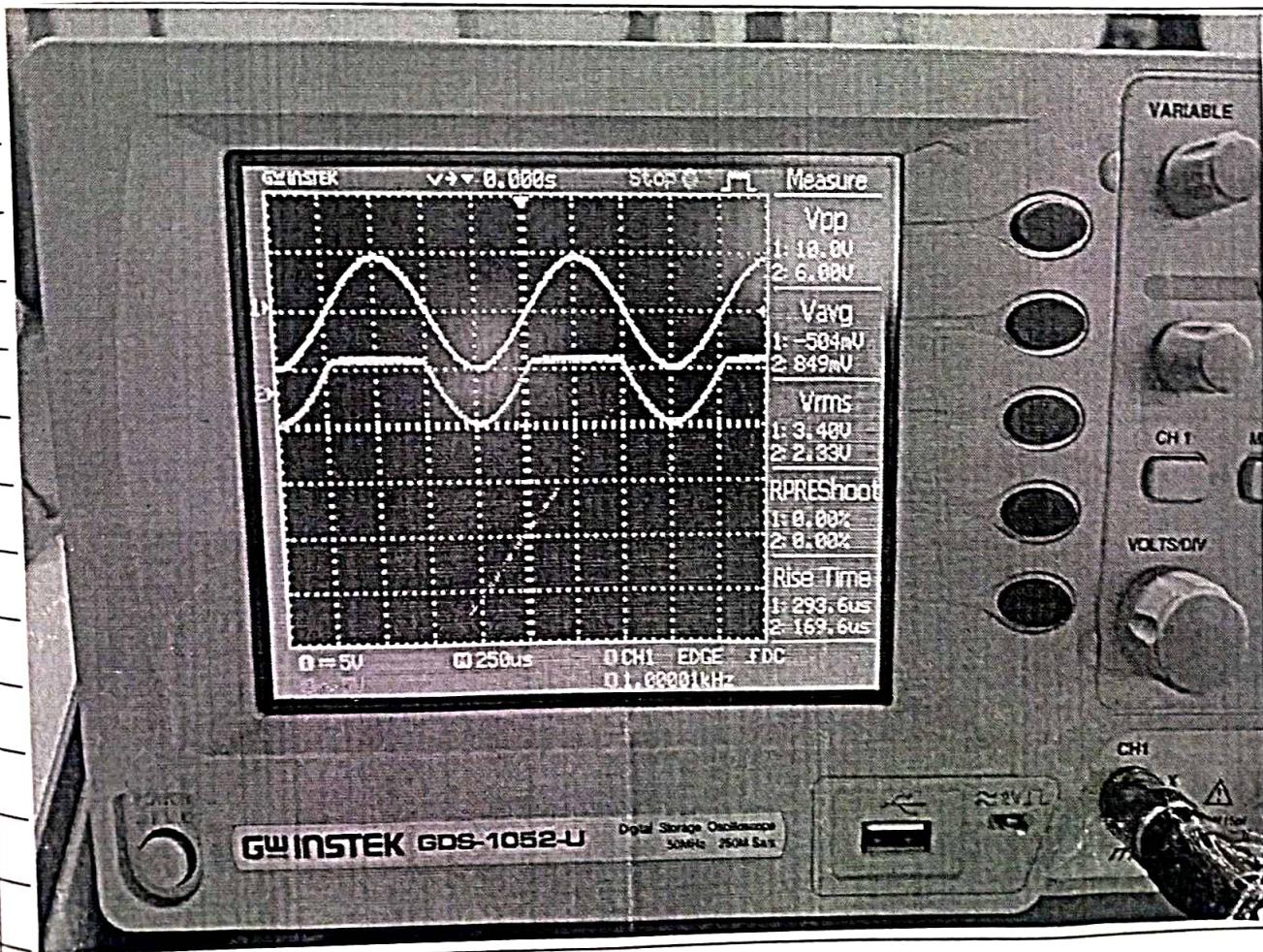
Theory - Circuit with which waveforms can be shaped by removing a portion of the signal is known as clipper circuit. They are used as limiters / slices to clip the waveform above / below a certain level.







Circuit Diagram.

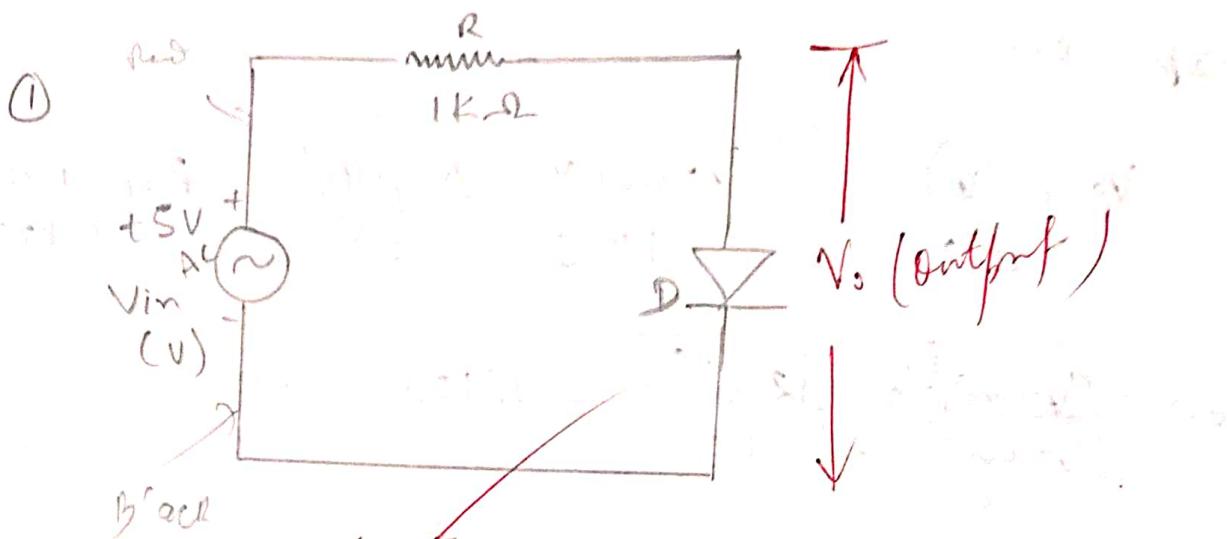

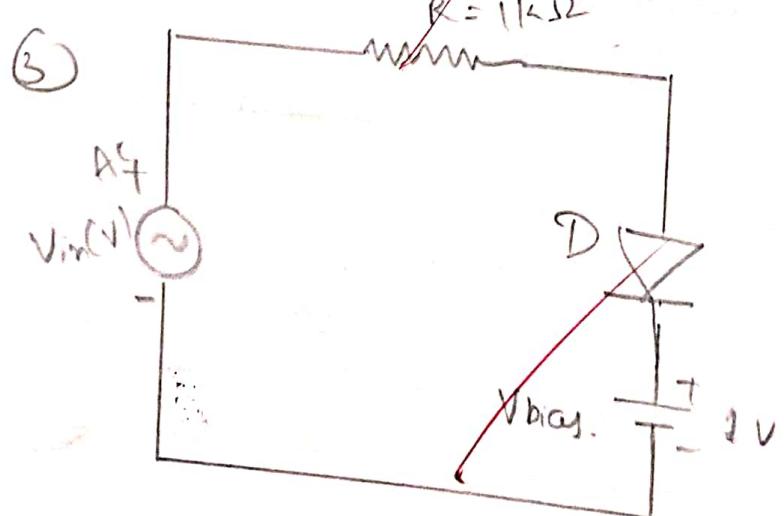
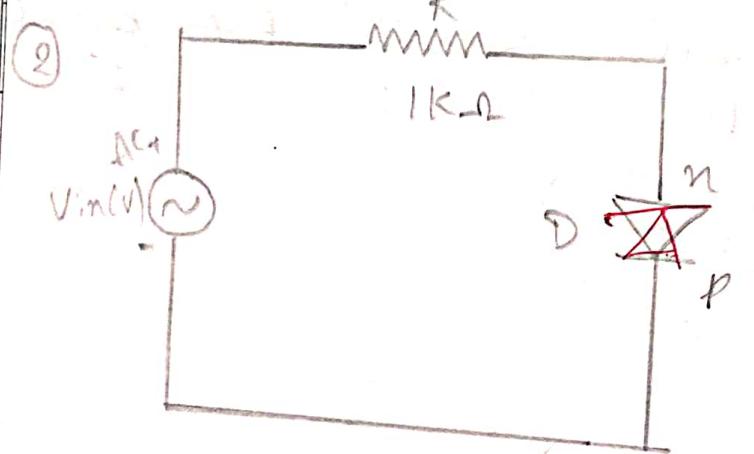
$6e - 0.3\text{ V}$
 $\text{Si} - 0.7\text{ V}$



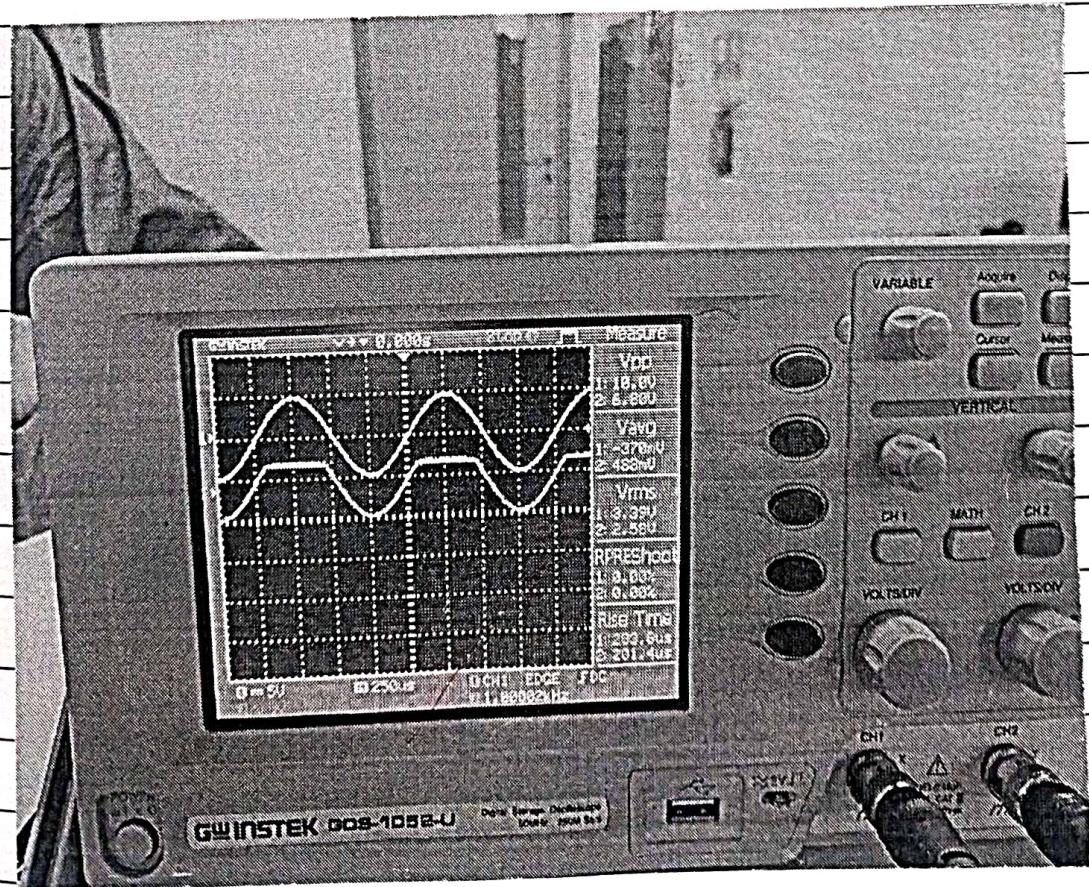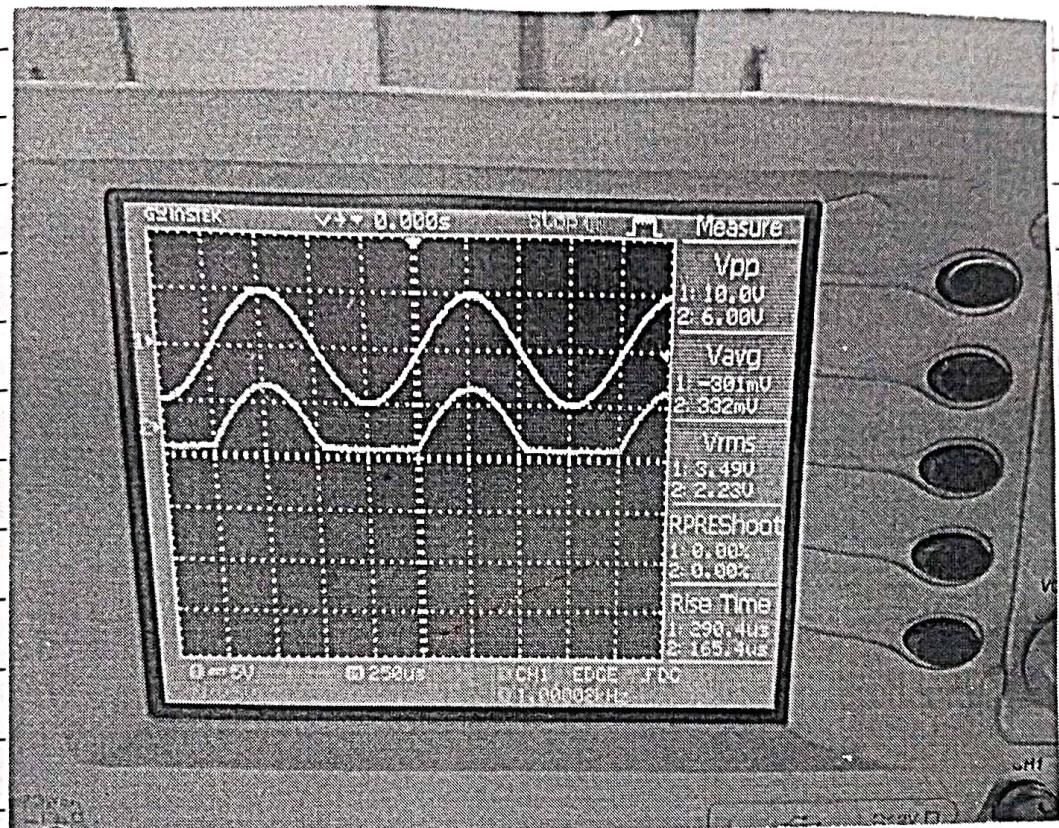

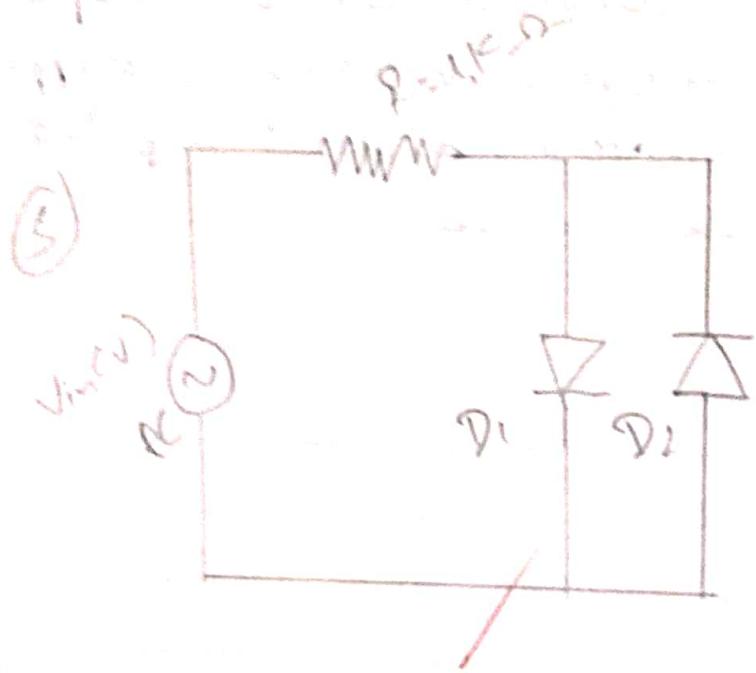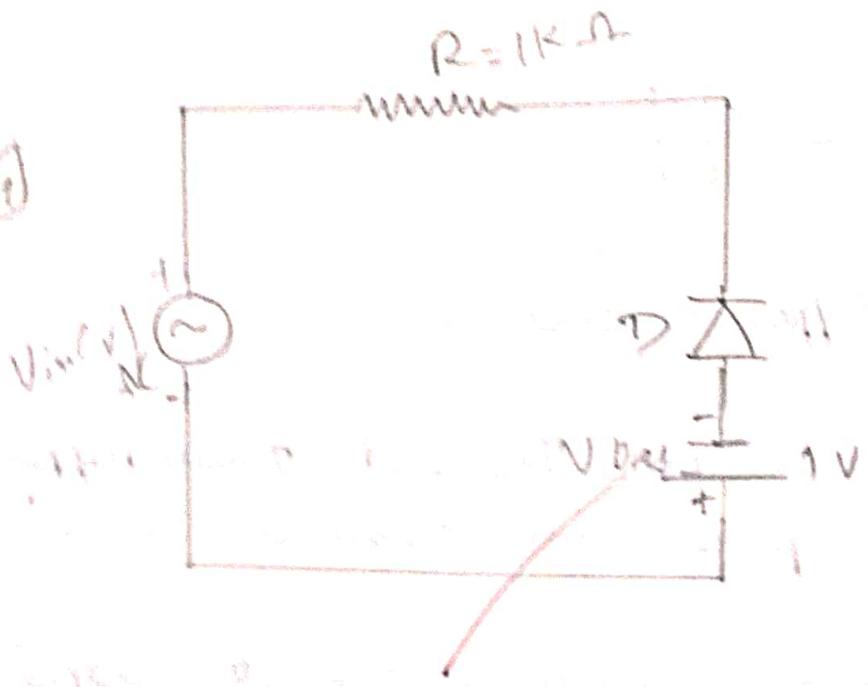

V848 NO. 22

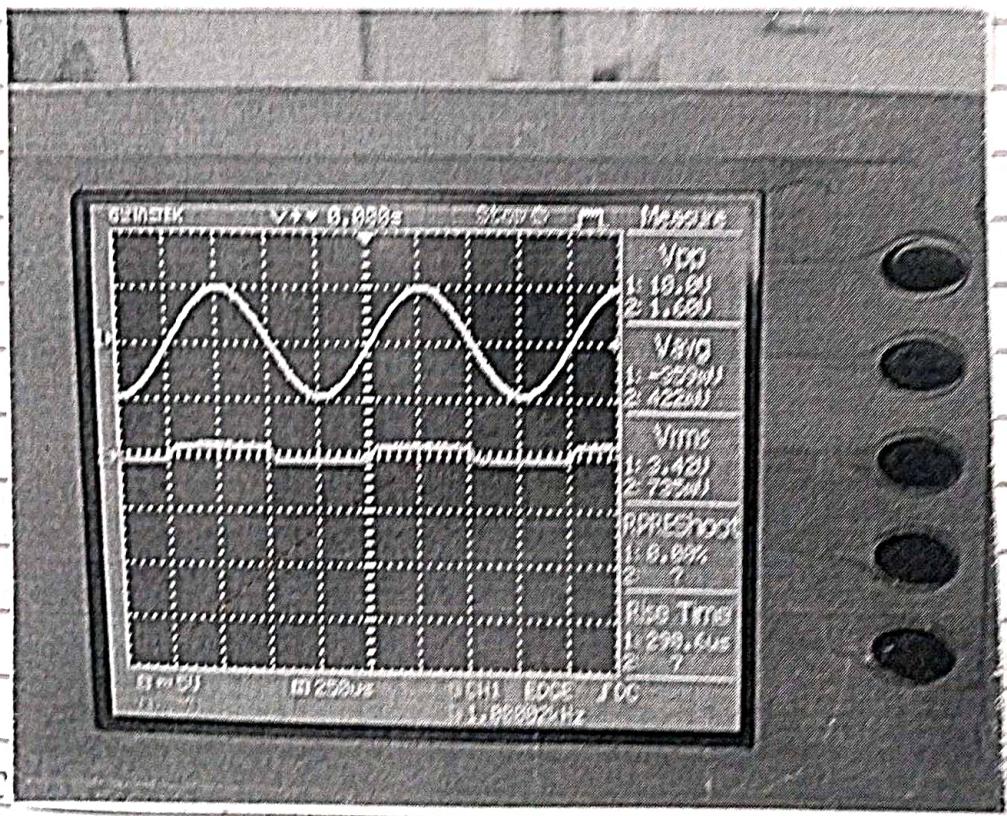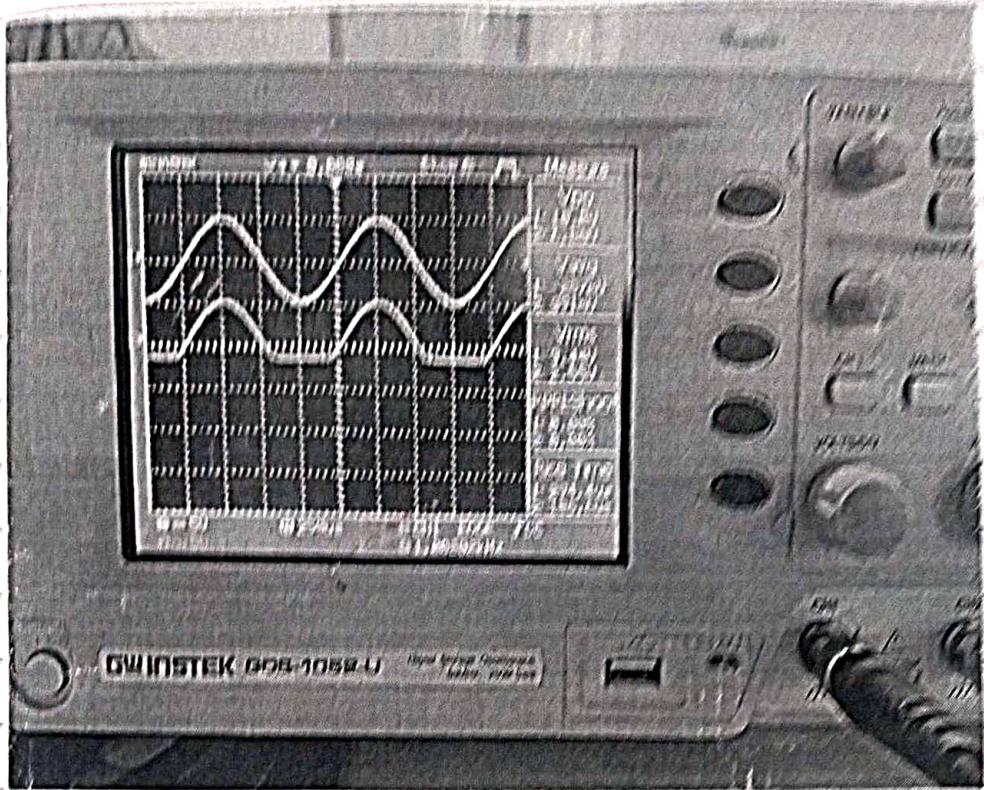

Rault

~~The clapper circuit using diode was addressed.~~


Teacher's Signature

Experiment - 12

dim
Study and perform Clamper circuit.





apparatus used



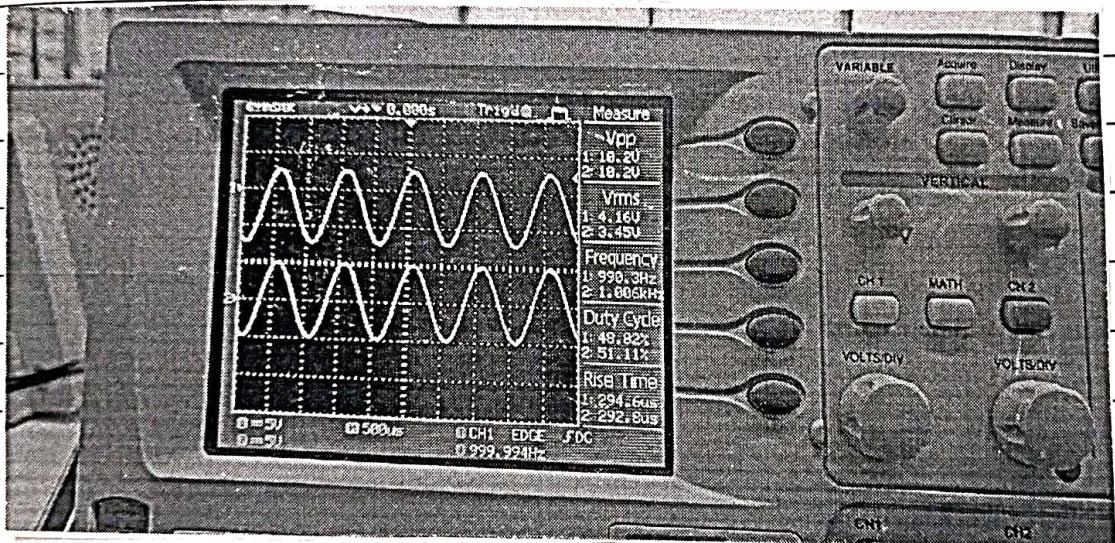
function generator, DSO, capacitors ($0.01\mu F$),
resistance ($10 M\Omega$), bread board, probe and
connecting wire.



Theory

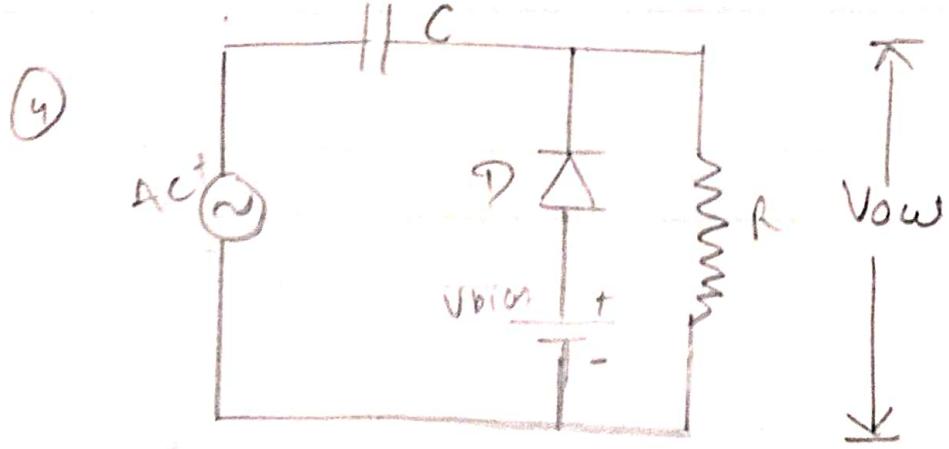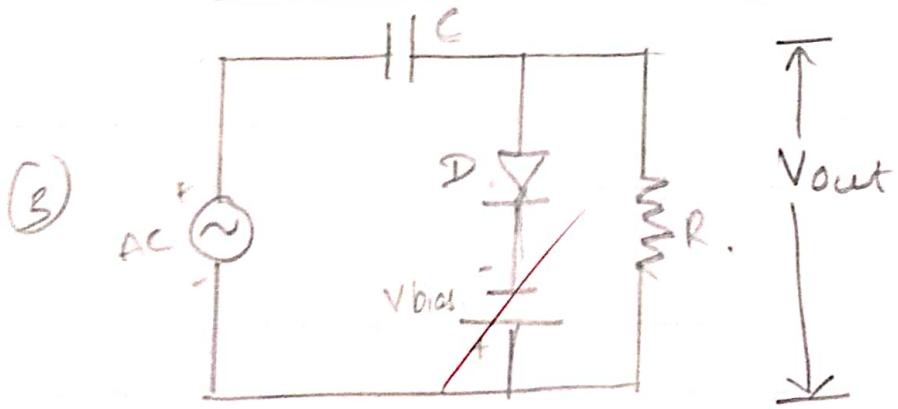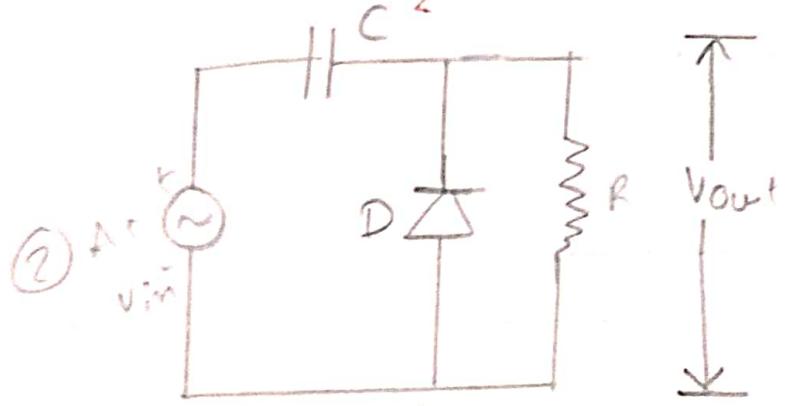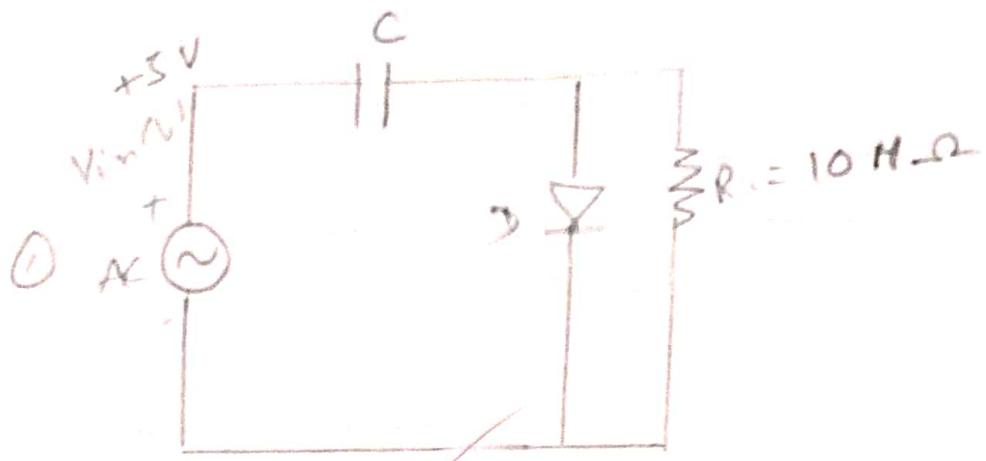Clamping circuit are used to change the dc levels of an alternating waveform without changing the shape of waveform. This is one more application of a diode circuit.



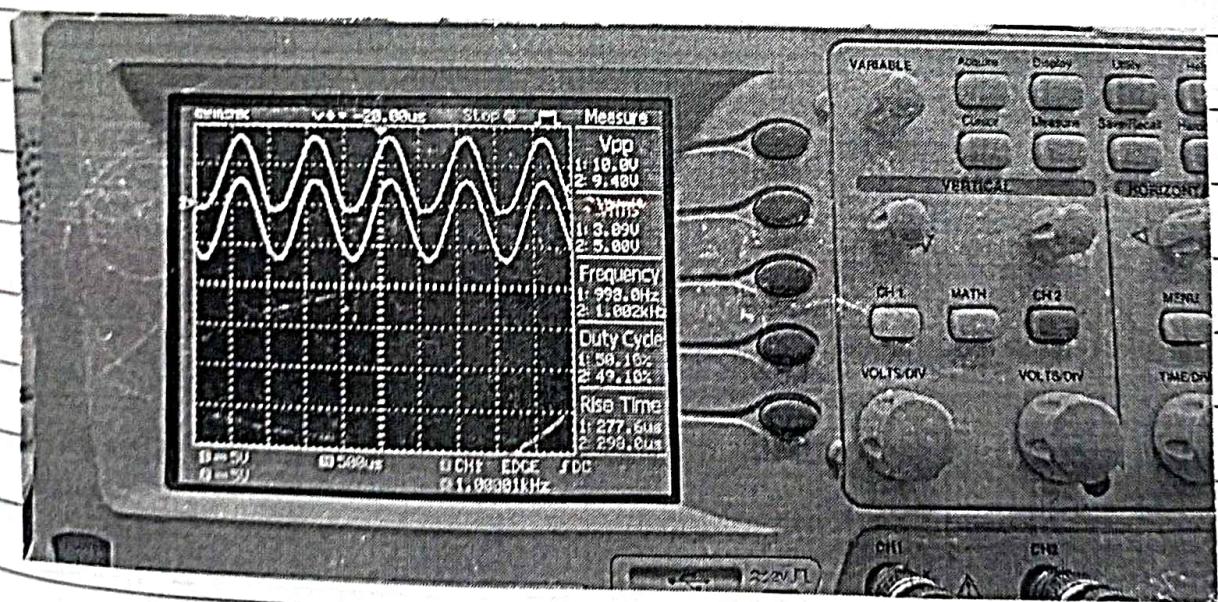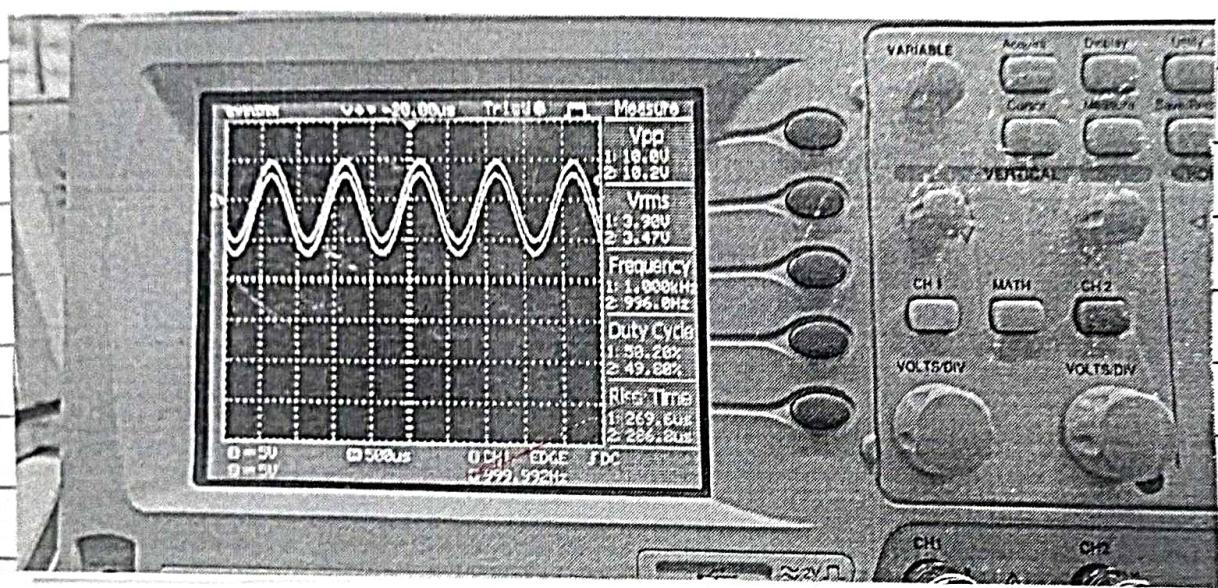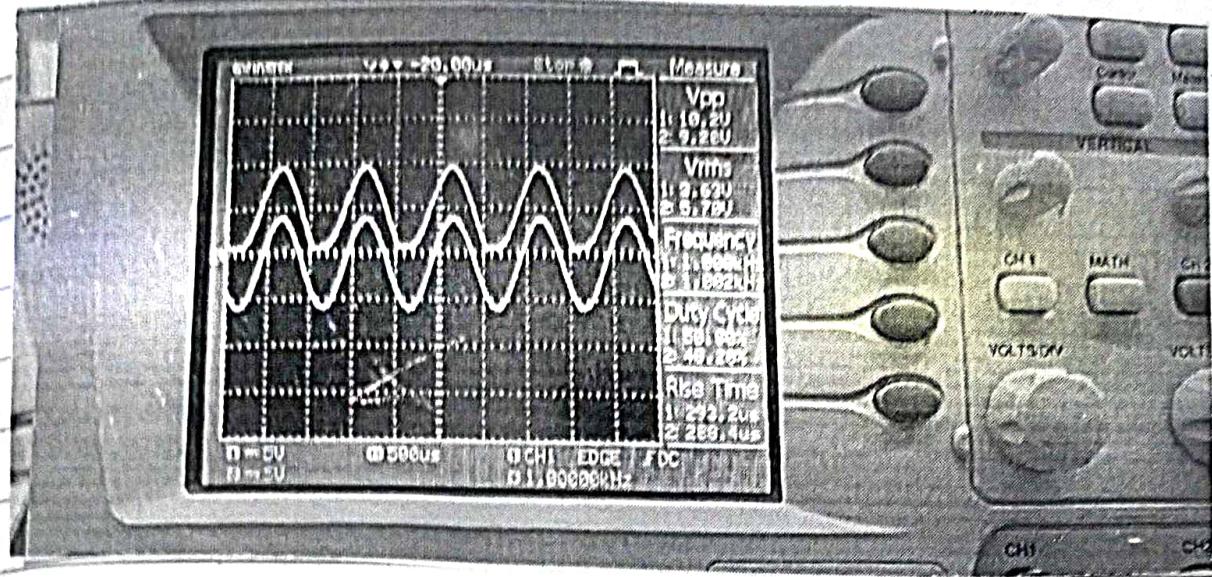

Result,

Circuit have been designed.

Waveform have been obtained.

1	Study of various measurement of equipment.	21/3/22	1
2.	Verification of ohm's law Kirchoff's current law and voltage law.	28/3/22	1
3.	To study and verification of Thvenin's Theorem.	11	4/4/22
4	Study and perform superposition theorem.	14	11/4/22
5	Verification of maxima power transfer theorem.	17	18/4/22
6	Study of Low Pass High Pass characteristics of RC filter circuit	21	25/4/22
7	To study and measurement of (I/V) (V-I) characteristic of p-n junction diode (Ge or Si)	25	21/5/22
8	① To study v-i characteristic of zener diode ② To study zener diode as voltage regulator	27	16/5/22
9	To design and study of half wave rectifiers	30	21/5/22
10	To design a bridge rectifiers circuit.	34	23/5/22

11 Design and study
clipper circuit

37

30

12 Study and perform
clamper circuit

40

30